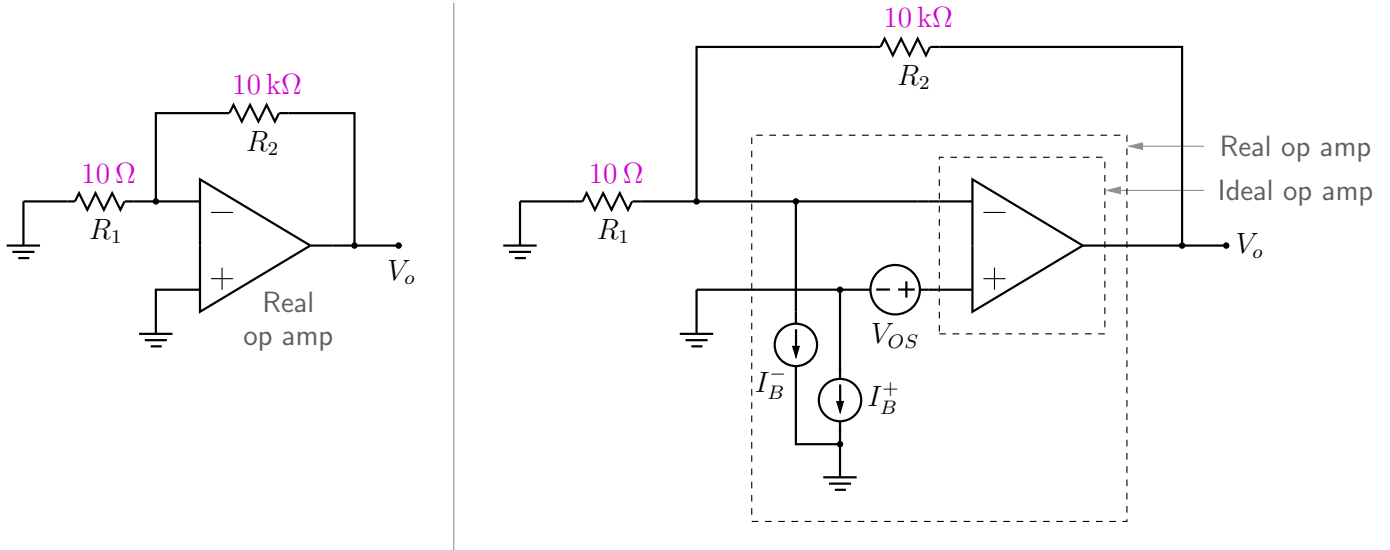


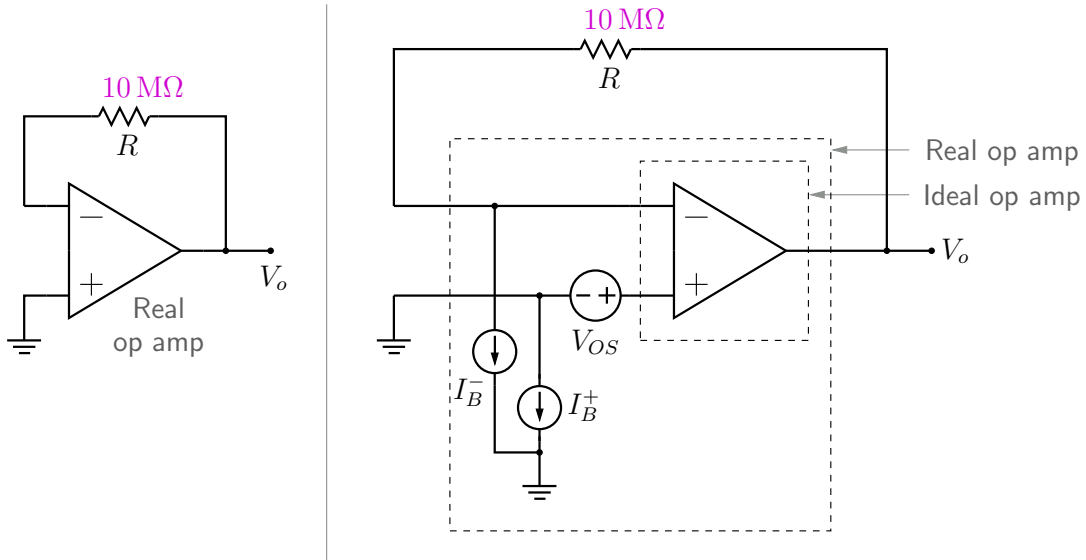
## 1 Measurement of Input Offset Voltage

Figure 1: Circuit for measurement of  $V_{OS}$ 

Now,

$$V_o = V_{OS} \left( 1 + \frac{R_2}{R_1} \right) + R_2 I_B^- \Rightarrow V_{OS} \approx \frac{V_o}{1 + \frac{R_2}{R_1}} \approx \frac{V_o}{\frac{R_2}{R_1}} = V_o \frac{R_1}{R_2}$$

## 2 Measurement of Input Bias Currents

Figure 2: Circuit for measurement of  $I_B^-$ 

Now,

$$V_o = V_{OS} + I_B^- R \Rightarrow V_{OS} \Rightarrow I_B^- \approx \frac{V_o}{R}$$

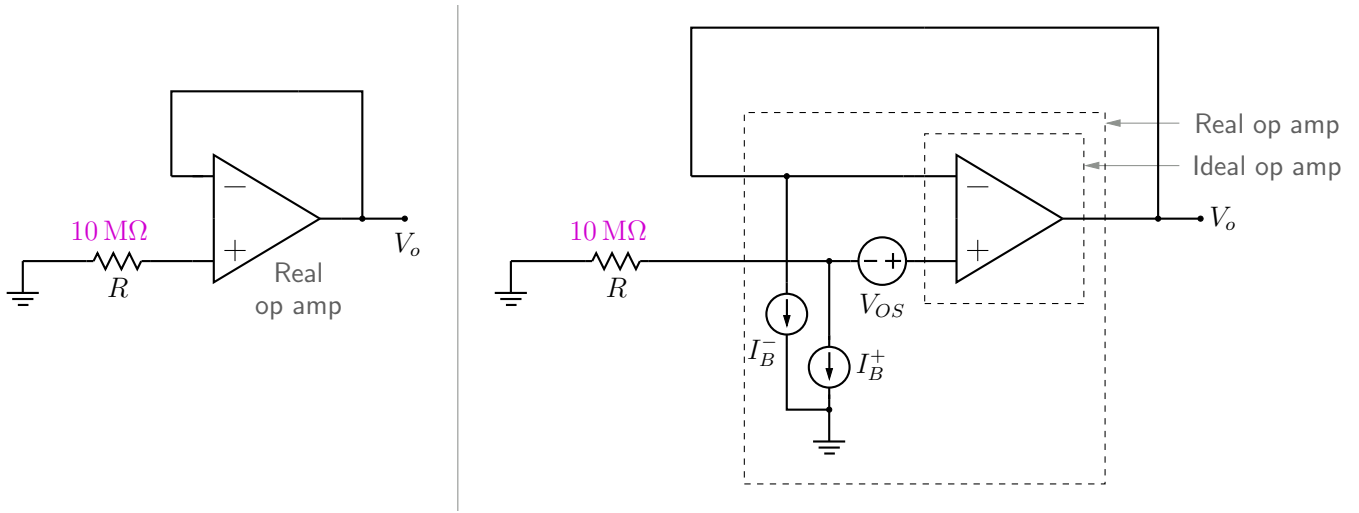


Figure 3: Circuit for measurement of  $I_B^+$

Now,

$$V_o = V_{OS} + I_B^+ R \Rightarrow V_{OS} \Rightarrow I_B^+ \approx \frac{V_o}{R}$$

So,

$$I_B = \frac{I_B^+ + I_B^-}{2} \quad I_{OS} = |I_B^+ - I_B^-|$$

## 2.1 Measurement of the Differential Voltage Gain, $A_d$

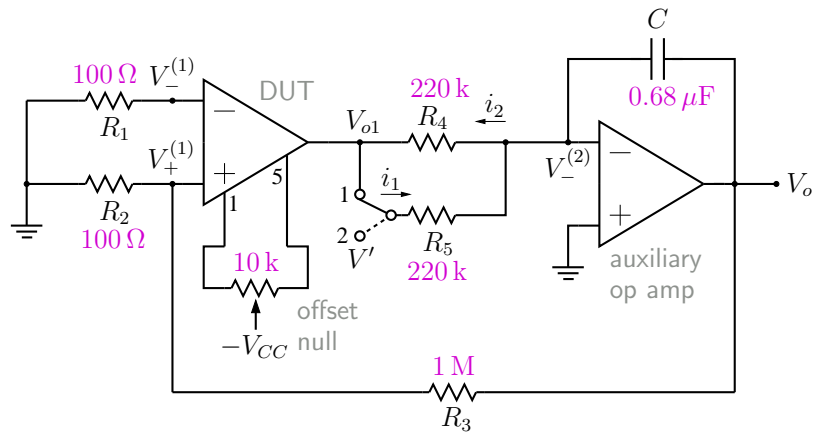


Figure 4: Circuit for measurement of  $A_{OL}$

- When switch is in position 1, minimise  $V_o$  by adjusting  $10k\Omega$  pot.
- When switch is in position 2,  $V_{o1}$  decreases by  $V' = 1V$  as the capacitor behaves like open circuit. Measure  $V_o$ , then

$$A_{OL} = -\frac{V'}{V_o} \cdot \frac{R_2 + R_3}{R_2} \approx -\frac{V'}{V_o} \frac{R_3}{R_2}$$

## 2.2 Learnings

Learnt to measure the DC parameters of a practical Opamp.

### 3 Comparison of popular op-amps

| Op-Amp | Input Offset Voltage | Input Bias Current | Input Offset Current | DC Open Loop Gain |
|--------|----------------------|--------------------|----------------------|-------------------|
| UA741C | $1mV$                | $80nA$             | $20nA$               | $200V/mV$         |
| TL084  | $3mV$                | $30pA$             | $5pA$                | $200V/mV$         |
| LM324  | $3mV$                | $20nA$             | $2nA$                | $100V/mV$         |

Table 3.1: Comparison of **Typical** Parameters (at  $25^{\circ}$ )

#### 3.1 Learnings

- UA741 has the lowest input offset voltage.
- TL084 has the lowest input bias current and offset current.
- UA741 and LM324 have the highest open loop gain.