

Figure 1: Three-Opamp Instrumentation Amplifier

1 Three-Opamp Instrumentation Amplifier using TL084

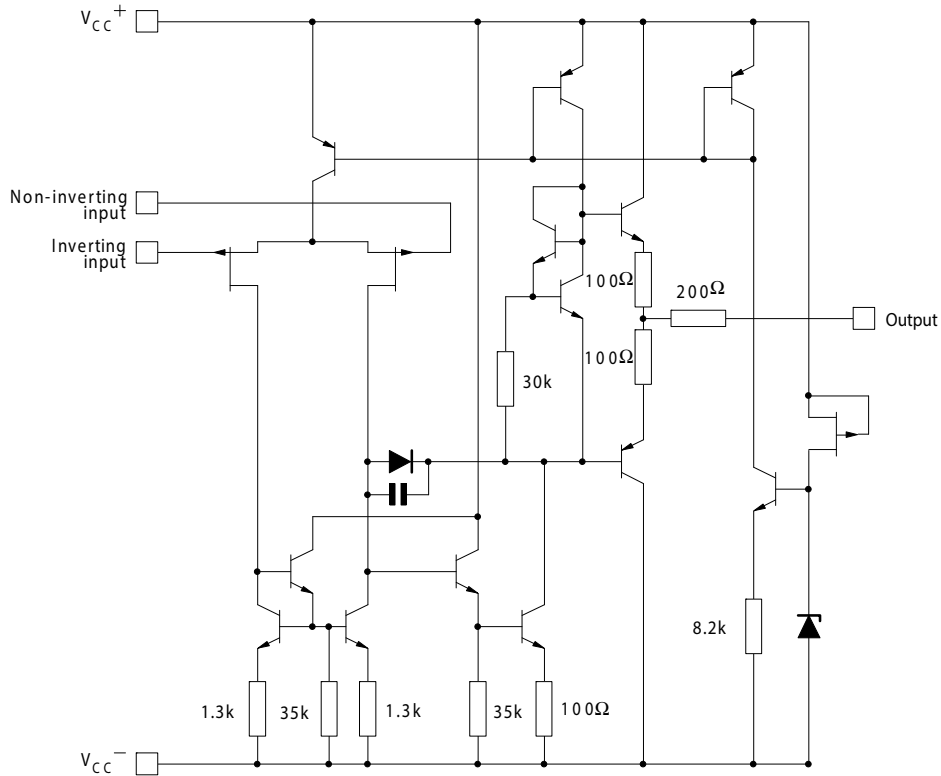


Figure 2: Circuit schematics TL084

$$A_d = \frac{V_{out}}{V_2 - V_1} = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_1} \right)$$

1.1 Measurement of the Differential Voltage Gain, A_d

$V_1 = 0, V_2 = 10 \sin(\omega t) mV, V_{CC} = 15V, -V_{CC} = -15V, R_1 = R_2 = 10k\Omega, R_3 = 1k\Omega, R_4 = 100k\Omega$

$$\text{Here, } A_d = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_1} \right) = \frac{100k}{1k} \left(1 + \frac{2 \cdot 10k}{10k} \right) = 300$$

$$V_{out} = V_2 \cdot A_d = 10m \cdot 300 = 3V$$

2 INA 128 Instrumentation Amplifier

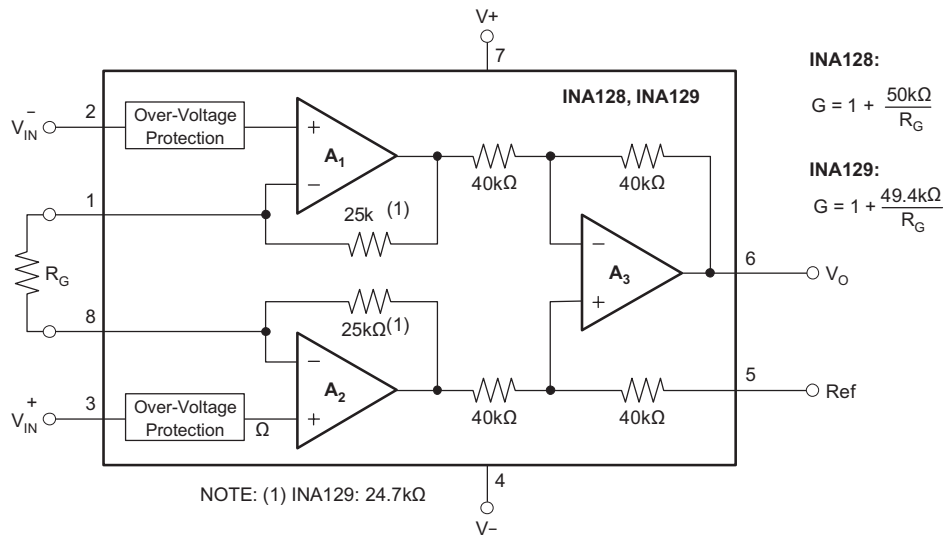


Figure 3: INA 128 Instrumentation Amplifier

$$A_d = \frac{V_{out}}{V_2 - V_1} = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_1} \right) = \left(1 + \frac{50k}{R_G} \right)$$

2.1 Measurement of the Differential Voltage Gain, A_d

$V_{in-} = 0$, $V_{in+} = 10 \sin(\omega t) mV$, $V_{CC} = 15V$, $-V_{CC} = -15V$, $R_G = 180\Omega$

Here, $A_d = \left(1 + \frac{50k}{R_G} \right) = \left(1 + \frac{50k}{180} \right) = 277.7$

$V_{out} = V_{in+} \cdot A_d = 10m \cdot 277.7 = 2.77V$

3 Questions

- i) In Sec 3.2 and 3.3, even under no-load conditions V_{out} was found to be non-zero. Give one or two reasons for this.
 - Under no-load conditions, the four gauges are at rest and so ideally $R_g = R_1 = R_2 = R_3 = R_4$, but due to tolerances of resistors this is not achieved and a small voltage difference is present which gets amplified by the op-amp.
 - Op-amp non idealities like input bias current, offset voltage also contribute to non-zero V_{out} .
- ii) Give two or three major advantages of the three-Opamp instrumentation amplifier as compared to the single-Opamp difference amplifier of Experiment 6.
 - A_d is easily changeable and can be set to higher values.
 - Higher differential input resistance.
 - High CMRR (due to high A_d and low A_{cm}).
- iii) Look at the data sheets of TL084 and INA128. Identify the major differences between these two ICs – i.e. Opamp parameters crucial for difference amplifier applications, such as the Loadcell application discussed in this experiment
 - INA128 has a higher CMRR (120dB) than TL084 (86dB)
 - TL084 has a lower input bias current ($20pA$) than INA128 ($5nA$)
 - INA128 has a lower offset voltage ($50\mu V$) than TL084 ($3mV$)
 - TL084 has a higher slew rate ($16V/\mu s$) than INA128 ($4V/\mu s$)
 - INA128 has a lower drift ($0.5\mu V/C^\circ$) than TL084 ($10\mu V/C^\circ$)
- iv) Identify one or two parameters of the INA128 that makes it superior to the TL084 based instrumentation amplifier.
 - INA128 is superior to TL084 in CMRR, offset voltage and drift
 - Additionally, INA128 has higher input voltage protection (40V) and lower noise (7 vs $15nV/\sqrt{Hz}$)

3.1 Learnings

Learnt the applications of instrumentation amplifiers, strain gages.