

# EE236: Experiment 5

## PMOS $I/V$ Characteristics and Applications

Param Rathour, 190070049  
Spring Semester, 2021-22

### Contents

<b>1</b>	<b>Overview of the experiment</b>	<b>2</b>
1.1	Aim of the experiment . . . . .	2
1.2	Methods . . . . .	2
<b>2</b>	<b>Design</b>	<b>2</b>
2.1	$I_D/V_{DS}$ Characteristics of PMOS . . . . .	3
2.2	$I_D/V_{GS}$ characteristics of PMOS for different $V_{DS}$ . . . . .	3
2.3	$I_D/V_{GS}$ characteristics of PMOS for different $V_{SB}$ . . . . .	3
<b>3</b>	<b>Simulation results</b>	<b>4</b>
3.1	Plots . . . . .	4
3.1.1	$I_D/V_{DS}$ characteristics of PMOS for different $V_{GS}$ . . . . .	4
3.1.2	$I_D/V_{GS}$ characteristics of PMOS for different $V_{DS}$ . . . . .	5
3.1.3	$I_D/V_{GS}$ characteristics of PMOS for different $V_{SB}$ . . . . .	6
3.2	NGSPICE Netlists . . . . .	7
3.2.1	$I_D/V_{DS}$ characteristics of PMOS for different $V_{GS}$ . . . . .	7
3.2.1.1	$V_{GS} = -2.5V$ . . . . .	7
3.2.1.2	$V_{GS} = -3V$ . . . . .	7
3.2.1.3	$V_{GS} = -3.5V$ . . . . .	7
3.2.1.4	$V_{GS} = -4V$ . . . . .	8
3.2.2	$I_D/V_{GS}$ characteristics of PMOS for different $V_{DS}$ . . . . .	8
3.2.2.1	$V_{DS} = -200mV$ . . . . .	8
3.2.2.2	$V_{DS} = -5V$ . . . . .	9
3.2.3	$I_D/V_{GS}$ characteristics of PMOS for different $V_{SB}$ . . . . .	9
3.2.3.1	$V_{SB} = 0$ . . . . .	9
3.2.3.2	$V_{SB} = -1V$ . . . . .	9
3.2.3.3	$V_{SB} = -2V$ . . . . .	10
3.2.3.4	$V_{SB} = -3V$ . . . . .	10
3.2.3.5	$V_{SB} = -4V$ . . . . .	11
3.3	Python Code for Plots and Calculations . . . . .	11
3.3.1	$I_D/V_{DS}$ characteristics of PMOS for different $V_{GS}$ . . . . .	11
3.3.2	$I_D/V_{GS}$ characteristics of PMOS for different $V_{DS}$ . . . . .	13
3.3.3	$I_D/V_{GS}$ characteristics of PMOS for different $V_{SB}$ . . . . .	16

# 1 Overview of the experiment

This report contains my approach to the experiment, the circuit's design with the relevant simulation code and output plots.

## 1.1 Aim of the experiment

- To plot and understand  $I_D/V_{DS}$  characteristics of PMOS at different  $V_{GS}$  and calculate  $r_{DS}$  (resistance linear region),  $r_0$  (resistance saturation region) and  $V_A$  (early voltage) considering channel length modulation.
- To plot and understand  $I_D/V_{GS}$  characteristics of PMOS in different regions and obtain the parameters  $V_T$ ,  $g_m$  and  $K$  (in  $mA/V^2$ )
- To plot and understand the effect of Body Bias on  $I_D/V_{GS}$  characteristics of PMOS and calculate  $\gamma$  (body effect coefficient)

## 1.2 Methods

First,  $I_D/V_{DS}$  characteristics of PMOS at different  $V_{GS}$  was plotted and the parameters were calculated & compared.

Then,  $I_D/V_{GS}$  characteristics of PMOS at was plotted in different regions by changing  $V_{DS}$  and the parameters were calculated.

Lastly,  $I_D/V_{GS}$  characteristics of PMOS at was plotted for different body voltage and behaviour of  $V_T$  versus  $V_{SB}$  was observed which was used to calculate body effect coefficient.

All parameters were calculated using python by exporting the vectors generated by NGSPICE.

# 2 Design

The common circuit designed for all parts is shown below

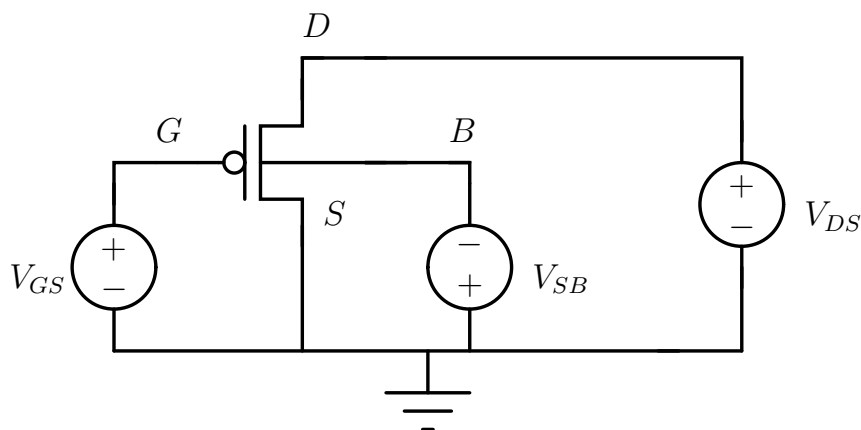


Figure 1: Circuit for I/V measurement

## 2.1 $I_D/V_{DS}$ Characteristics of PMOS

For the first part the Voltage  $V_{GS}$  was varied from  $-2.5V$  to  $-4V$  in steps of  $-0.5V$ .

For each  $V_{GS}$ ,  $V_{DS}$  was varied from 0 to  $-5V$

As in linear region slope  $I_D/V_{DS}$  is maximum  $\rightarrow r_{DS} = \frac{1}{\text{maximum slope}}$

Similarly in saturation region slope  $I_D/V_{DS}$  is minimum  $\rightarrow r_0 = \frac{1}{\text{minimum slope}}$

Early voltage can be calculated by taking the mean of the  $x$ -intercepts of the extrapolated lines from saturation regions.

$$x - \text{intercept} = \frac{-(y - \text{intercept})}{\text{slope}}$$

and slope,  $y$ -intercepts were calculated using Python's `Scipy` package This graph is a straight line in some range of  $I, V$ . Also,  $I_L = 0$  for Dark characteristics.

We can calculate its slope to get  $\eta$  and  $y$ -intercept by interpolating that straight line.

## 2.2 $I_D/V_{GS}$ characteristics of PMOS for different $V_{DS}$

Again, the above circuit was used (Figure 1),  $V_{GS}$  was varied from 0 to  $-5V$

$$I_D = \frac{1}{2}K(2(V_{GS} - V_T)V_{DS} - (V_{DS})^2)$$

In linear region,  $(V_{DS})^2$  can be ignored (as  $V_{DS} = -200mV$ ) to give

$$I_D = K(V_{GS} - V_T)V_{DS}$$

So  $V_T = -\underbrace{(y - \text{intercept})}_{-K \cdot V_T \cdot V_{DS}} / \underbrace{\text{slope}}_{K \cdot V_{DS}}$  and  $g_m = \frac{\partial I_D}{\partial V_{GS}} = \frac{I_D}{V_{GS}}$  (as the plot is linear)

In saturation region, as  $V_{DS} = -5V \leq (V_{GS} - V_T)$ ,  $I_D$  depends only on  $(V_{GS} - V_T)$  (ideally)

$$I_D = \frac{1}{2}K(V_{GS} - V_T)^2$$

$$\sqrt{I_D} = \frac{1}{\sqrt{2}}\sqrt{K}(V_{GS} - V_T)$$

So from the  $\sqrt{I_D}/V_{GS}$  characteristics,  $K = 2 \cdot \text{slope}^2$  (in  $A/V^2$ ) =  $1000 \cdot 2 \cdot \text{slope}^2$  (in  $mA/V^2$ )

$$V_T = -\underbrace{(y - \text{intercept})}_{-\frac{1}{\sqrt{2}}\sqrt{K} \cdot V_T} / \underbrace{\text{slope}}_{\frac{1}{\sqrt{2}}\sqrt{K}}$$

and  $g_m = \frac{\partial I_D}{\partial V_{GS}}$  will be different for different  $V_{GS}$  (as the plot is quadratic)

Say,  $V_{GS} = -3V$ , then at that point,  $g_m = \frac{I_D}{V_{GS}} \mathcal{U}$

## 2.3 $I_D/V_{GS}$ characteristics of PMOS for different $V_{SB}$

Again, the same circuit ((Figure 1)) was used.

With  $V_{SB}$  varying from 0 to  $-4V$  in steps of  $-1V$ .  $V_{DS} = -200mV$

To calculate  $V_T$ , again we extrapolate the lines and get the  $x$ -intercept.

Then  $\gamma$  was calculated for each  $V_T$  and  $V_{SB}$  as shown below (average of all  $\gamma$  was taken)

$$V_T = V_{T0} + \gamma(\sqrt{\varphi_s - V_{SB}} - \sqrt{\varphi_s}) \quad (\text{where } \varphi_s = 0.8V)$$


### 3 Simulation results

#### 3.1 Plots


##### 3.1.1 $I_D/V_{DS}$ characteristics of PMOS for different $V_{GS}$

$V_{GS}$ (in V)	$R_{DS}$ (in $\Omega$ )	$V_A$ (in V)	$R_0$ (in $\Omega$ )
-2.5	2984.17	32.89471976	116548.76
-3	2298.15	32.8947267	69217.08
-3.5	1868.59	32.89473013	45799.08
-4	1574.32	32.89436244	32528.79


Table 1: Parameter Values obtained from the characteristics

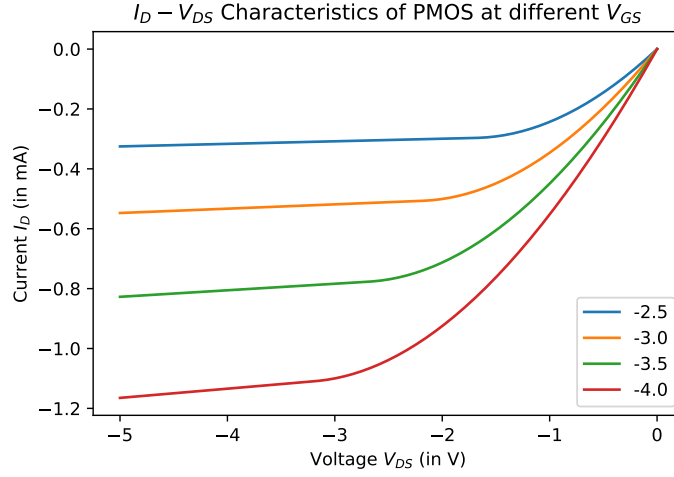

(a) Different  $V_{GS}$

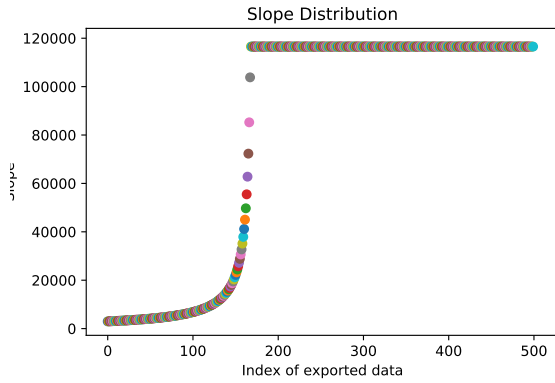

(b) Slope Distribution

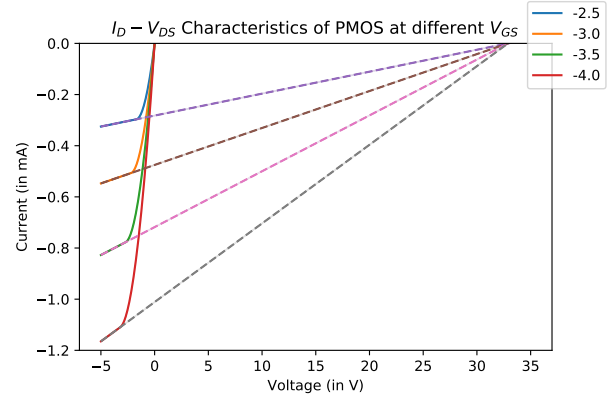


(c) Characteristics with the Extrapolated Lines


Figure 2:  $I_D/V_{DS}$  characteristics of PMOS

In Figure 2, as magnitude of  $V_{GS}$  increases, magnitude of  $I_D$  increases. All extrapolated lines meet at  $V_A = 32.89463475487444V$

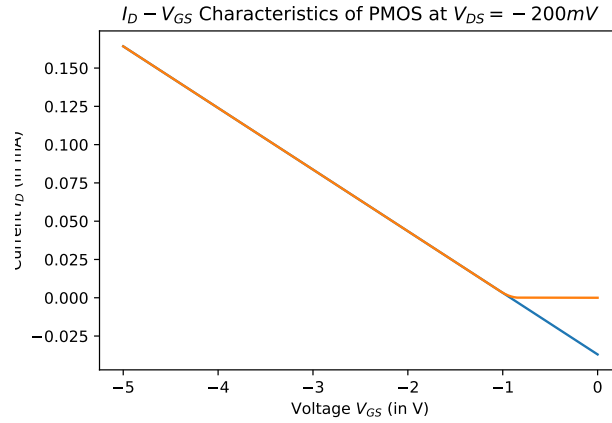
### 3.1.2 $I_D/V_{GS}$ characteristics of PMOS for different $V_{DS}$



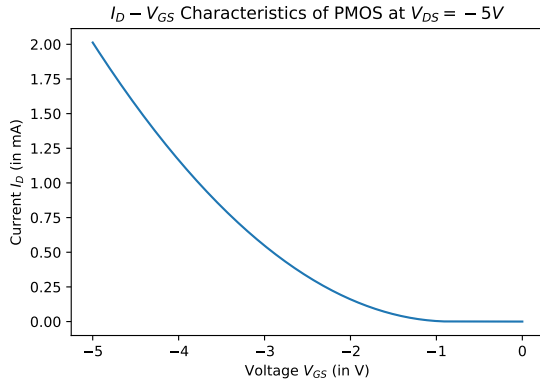(a)  $V_{DS} = -200mV$  with the Extrapolated Line



(b)  $V_{DS} = -5mV$

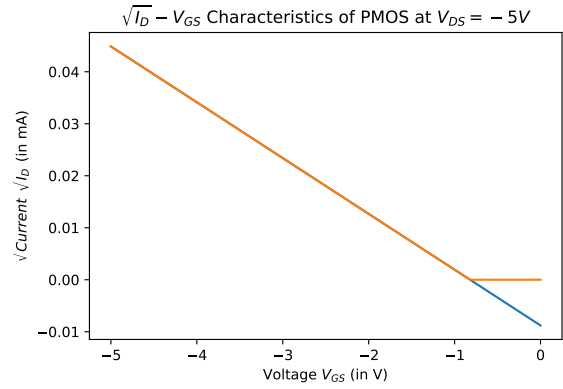

(c)  $\sqrt{I_D}/V_{GS}$  characteristics when  $V_{DS} = -5V$  with the Extrapolated Line

Figure 3:  $I_D/V_{GS}$  characteristics of PMOS

In Figure 3a), as magnitude of  $V_{GS}$  increases (neglecting the small  $V_{GS}$  values as PMOS is saturated), magnitude of  $I_D$  increases linearly giving

$$V_T = -0.92V \text{ and } g_m = -0.0402432m\mathcal{U}$$

In Figure 3b), as magnitude of  $V_{GS}$  increases (neglecting the small  $V_{GS}$  values as PMOS is not saturated), magnitude of  $I_D$  increases quadratically giving

$$V_T = -0.82V, g_m = -0.503424m\mathcal{U} \text{ and } K = 0.2304mA/V^2$$

### 3.1.3 $I_D/V_{GS}$ characteristics of PMOS for different $V_{SB}$

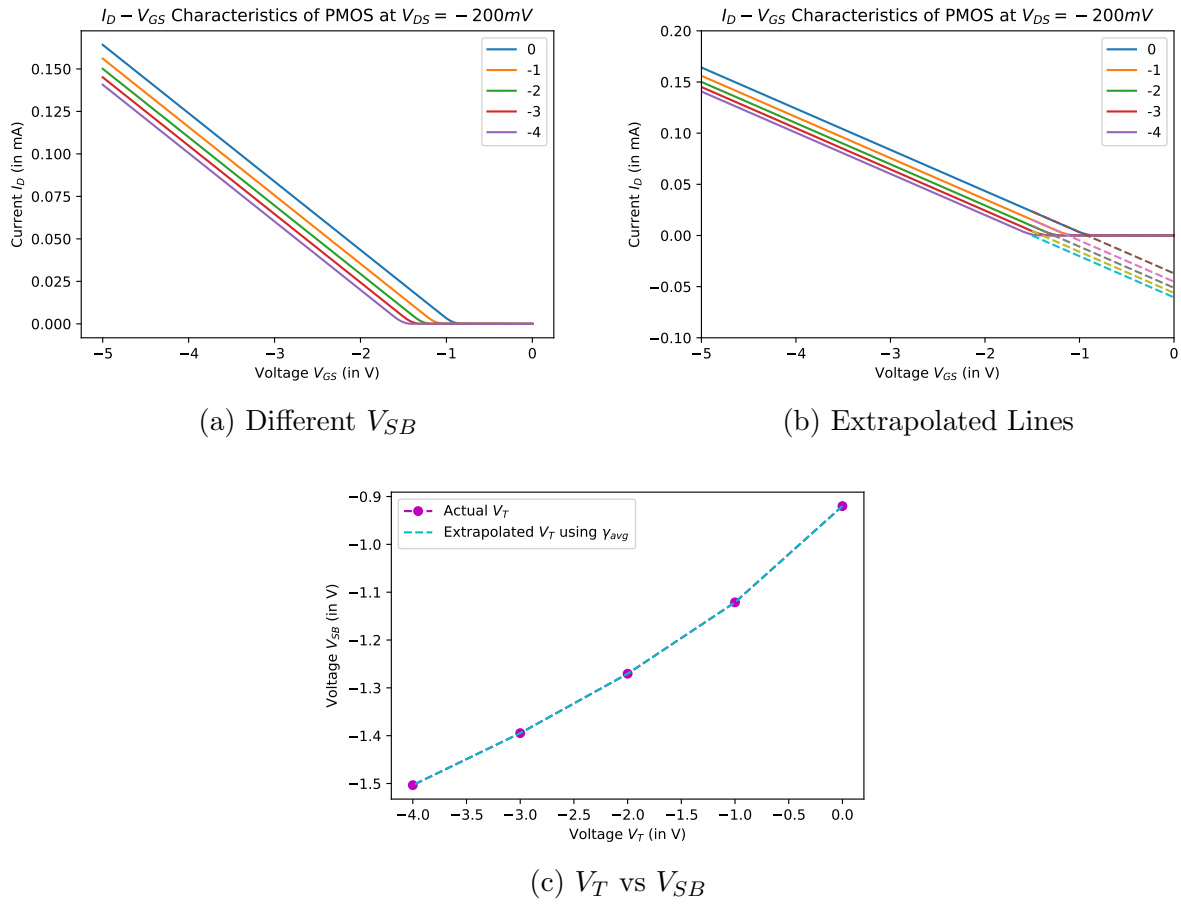


Figure 4:  $I_D/V_{GS}$  characteristics of PMOS

In Figure 4, as magnitude of  $V_{SB}$  increases, magnitude of  $I_D$  reduces giving  $V_T = -0.92V, -1.1212461V, -1.27050172V, -1.39471918V, -1.50340825V$  for  $V_{SB} = 0V, -1V, -2V, -3V, -4V$  respectively.

From these values, we get  $\gamma = -0.45\sqrt{V}$  and it fits the original curve very well.

The dependence of  $V_T$  on  $V_{SB}$  is similar to a square root graph which increases very slowly. As magnitude of  $V_T$  increases,  $V_{SB}$ 's magnitude decreases.

## 3.2 NGSPICE Netlists

### 3.2.1 $I_D/V_{DS}$ characteristics of PMOS for different $V_{GS}$

#### 3.2.1.1 $V_{GS} = -2.5V$

```
Param Rathour (190070049), I_D - V_DS Characteristics of PMOS at V_GS = -2.5V
.include pmos.txt ; Includes PMOS Model
M1 d g gnd gnd ALD1107
VD mid gnd 0
Vdummy d mid 0
VG g gnd -2.5
.dc VD 0 -5 -0.01 ; DC Analysis
.control
run
let I_D = -I(Vdummy)
let V_DS = V(d)
plot I_D vs V_DS
wrdata 111.txt I_D vs V_DS
.endc
.end
```

#### 3.2.1.2 $V_{GS} = -3V$

```
Param Rathour (190070049), I_D - V_DS Characteristics of PMOS at V_GS = -3V
.include pmos.txt ; Includes PMOS Model
M1 d g gnd gnd ALD1107
VD mid gnd 0
Vdummy d mid 0
VG g gnd -3
.dc VD 0 -5 -0.01 ; DC Analysis
.control
run
let I_D = -I(Vdummy)
let V_DS = V(d)
plot I_D vs V_DS
wrdata 112.txt I_D vs V_DS
.endc
.end
```

#### 3.2.1.3 $V_{GS} = -3.5V$

```
Param Rathour (190070049), I_D - V_DS Characteristics of PMOS at V_GS = -3.5V
.include pmos.txt ; Includes PMOS Model
M1 d g gnd gnd ALD1107
VD mid gnd 0
```

```

Vdummy d mid 0
VG g gnd -3.5
.dc VD 0 -5 -0.01          ; DC Analysis
.control
run
let I_D = -I(Vdummy)
let V_DS = V(d)
plot I_D vs V_DS
wrdata 113.txt I_D vs V_DS
.endc
.end

```

#### 3.2.1.4 $V_{GS} = -4V$

```

Param Rathour (190070049), I_D - V_DS Characteristics of PMOS at V_GS = -4V
.include pmos.txt ; Includes PMOS Model
M1 d g gnd gnd ALD1107
VD mid gnd 0
Vdummy d mid 0
VG g gnd -4
.dc VD 0 -5 -0.01          ; DC Analysis
.control
run
let I_D = -I(Vdummy)
let V_DS = V(d)
plot I_D vs V_DS
wrdata 114.txt I_D vs V_DS
.endc
.end

```

### 3.2.2 $I_D/V_{GS}$ characteristics of PMOS for different $V_{DS}$

#### 3.2.2.1 $V_{DS} = -200mV$

```

Param Rathour (190070049), I_D - V_GS Characteristics of PMOS at V_DS = -200mV
.include pmos.txt ; Includes PMOS Model
M1 d g gnd gnd ALD1107
VD mid gnd -200m
Vdummy d mid 0
VG g gnd 0
.dc VG 0 -5 -0.01          ; DC Analysis
.control
run
let I_D = I(Vdummy)
let V_GS = V(g)
plot I_D vs V_GS

```



```
wrdata 211.txt I_D vs V_GS
.endc
.end
```

### 3.2.2.2 $V_{DS} = -5V$

```
Param Rathour (190070049), I_D - V_GS Characteristics of PMOS at V_DS = -5V
.include pmos.txt ; Includes PMOS Model
M1 d g gnd gnd ALD1107
VD mid gnd -5
Vdummy d mid 0
VG g gnd 0
.dc VG 0 -5 -0.01 ; DC Analysis
.control
run
let I_D = I(Vdummy)
let V_GS = V(g)
plot sqrt(I_D) vs V_GS
wrdata 221.txt I_D vs V_GS
.endc
.end
```

### 3.2.3 $I_D/V_{GS}$ characteristics of PMOS for different $V_{SB}$

#### 3.2.3.1 $V_{SB} = 0$

```
Param Rathour (190070049), Effect of Body Bias
.include pmos.txt ; Includes PMOS Model
M1 d g gnd b ALD1107
VD mid gnd -200m
Vdummy d mid 0
VG g gnd 0
VB b gnd 0
.dc VG 0 -5 -0.01 ; DC Analysis
.control
run
let I_D = I(Vdummy)
let V_GS = V(g)
plot I_D vs V_GS
wrdata 312.txt I_D vs V_GS
.endc
.end
```

#### 3.2.3.2 $V_{SB} = -1V$

```

Param Rathour (190070049), Effect of Body Bias
.include pmos.txt ; Includes PMOS Model
M1 d g gnd b ALD1107
VD mid gnd -200m
Vdummy d mid 0
VG g gnd 0
VB b gnd 1
.dc VG 0 -5 -0.01 ; DC Analysis
.control
run
let I_D = I(Vdummy)
let V_GS = V(g)
plot I_D vs V_GS
wrdata 312.txt I_D vs V_GS
.endc
.end

```

### 3.2.3.3 $V_{SB} = -2V$

```

Param Rathour (190070049), Effect of Body Bias
.include pmos.txt ; Includes PMOS Model
M1 d g gnd b ALD1107
VD mid gnd -200m
Vdummy d mid 0
VG g gnd 0
VB b gnd 2
.dc VG 0 -5 -0.01 ; DC Analysis
.control
run
let I_D = I(Vdummy)
let V_GS = V(g)
plot I_D vs V_GS
wrdata 313.txt I_D vs V_GS
.endc
.end

```

### 3.2.3.4 $V_{SB} = -3V$

```

Param Rathour (190070049), Effect of Body Bias
.include pmos.txt ; Includes PMOS Model
M1 d g gnd b ALD1107
VD mid gnd -200m
Vdummy d mid 0
VG g gnd 0

```

```

VB b gnd 3
.dc VG 0 -5 -0.01          ; DC Analysis
.control
run
let I_D = I(Vdummy)
let V_GS = V(g)
plot I_D vs V_GS
wrdata 314.txt I_D vs V_GS
.endc
.end

```

### 3.2.3.5 $V_{SB} = -4V$

```

Param Rathour (190070049), Effect of Body Bias
.include pmos.txt ; Includes PMOS Model
M1 d g gnd b ALD1107
VD mid gnd -200m
Vdummy d mid 0
VG g gnd 0
VB b gnd 4
.dc VG 0 -5 -0.01          ; DC Analysis
.control
run
let I_D = I(Vdummy)
let V_GS = V(g)
plot I_D vs V_GS
wrdata 315.txt I_D vs V_GS
.endc
.end

```

## 3.3 Python Code for Plots and Calculations

```

import numpy as np
import matplotlib.pyplot as plt
from scipy import stats
import math
import pandas as pd
import bisect

```

### 3.3.1 $I_D/V_{DS}$ characteristics of PMOS for different $V_{GS}$

```

V_GS = np.arange(-2.5,-4.5,-0.5)

V_DS = []
I_D = []

```

```

fig1, ax1 = plt.subplots()
ax1.set_xlabel('Voltage $V_{DS}$ (in V)')
ax1.set_ylabel('Current $I_D$ (in mA)')
ax1.set_title('$I_D$-$V_{DS}$ Characteristics of PMOS at different $V_{GS}$')

for i in range(len(V_GS)):
    data = pd.read_csv('E:\Program_Files\Spice64\EE236\Lab5\\11' + str(i+1)
        + '.txt', header = None, skipinitialspace=True, delim_whitespace=True)
    V_DS.append(data[0])
    I_D.append(data[1])
    ax1.plot(V_DS[i], 1000*I_D[i], '-o', markersize=0.01)
ax1.legend(V_GS)
fig1.set_dpi(150)
fig1.savefig('111.pdf')

slopes = []
for i in range(len(V_GS)):
    slope = []
    for j in range(len(V_DS[i])-1):
        slope.append((I_D[i][j+1]-I_D[i][j])/(V_DS[i][j+1]-V_DS[i][j]))
    slopes.append(slope)
# slopes[0]

slope_min = np.zeros(len(V_GS))
slope_max = np.zeros(len(V_GS))
for i in range(len(V_GS)):
    slope_min[i] = min(slopes[i])
    slope_max[i] = max(slopes[i])
print(slope_min)
print(slope_max)

r_DS = [1/i for i in slope_max]
print("r_DS", r_DS)
r_0 = [1/i for i in slope_min]
print("r_0", r_0)

fig1, ax1 = plt.subplots()
ax1.set_xlabel('Index of exported data')
ax1.set_ylabel('Slope')
ax1.set_title('Slope Distribution')
for i in range(len(V_DS[0])-1):
    plt.scatter(i, (V_DS[0][i+1]-V_DS[0][i])/(I_D[0][i+1]-I_D[0][i]))
fig1.set_dpi(150)
fig1.savefig('121.pdf')

y_intercepts = np.zeros(len(V_GS))

```

```

slope_fit = np.zeros(len(V_GS))
for i in range(len(V_GS)):
    slope, intercept, r_value, p_value, std_err =
    stats.linregress(V_DS[i][-2:], I_D[i][-2:])
    y_intercepts[i] = intercept
    slope_fit[i] = slope
print(slope_fit)
print(y_intercepts)

V_A = np.zeros(len(V_GS))
R_0 = np.zeros(len(V_GS))
fig1, ax1 = plt.subplots()
ax1.set_xlabel('Voltage (in V)')
ax1.set_ylabel('Current (in mA)')
ax1.set_ylim([-1.2,0])
ax1.set_title('$I_D-V_{DS}$ Characteristics of PMOS at different $V_{GS}$')
fig1.set_dpi(150)
intersect = 35
x = np.arange(-5,intersect,0.01)
for i in range(len(V_GS)):
    ax1.plot(x, 1000*(slope_fit[i]*x+y_intercepts[i]), '--o',
    markersize=0.01)
    ax1.plot(V_DS[i], 1000*I_D[i], '-o', markersize=0.01)
    V_A[i] = -y_intercepts[i]/slope_fit[i]
    R_0[i] = 1/slope_fit[i]
print(V_A)
print(np.mean(V_A))
print(R_0)
fig1.savefig('122.pdf')

```

### 3.3.2 $I_D/V_{GS}$ characteristics of PMOS for different $V_{DS}$

```

slopes = []
for i in range(len(V_GS)):
    slope = []
    for j in range(len(V_DS[i])-1):
        slope.append((I_D[i][j+1]-I_D[i][j])/(V_DS[i][j+1]-V_DS[i][j]))
    slopes.append(slope)
# slopes[0]

slope_min = np.zeros(len(V_GS))
slope_max = np.zeros(len(V_GS))
for i in range(len(V_GS)):
    slope_min[i] = min(slopes[i])
    slope_max[i] = max(slopes[i])
print(slope_min)

```

```

print(slope_max)

r_DS = [1/i for i in slope_max]
print("r_DS", r_DS)
r_0= [1/i for i in slope_min]
print("r_0", r_0)

fig1, ax1 = plt.subplots()
ax1.set_xlabel('Index of exported data')
ax1.set_ylabel('Slope')
ax1.set_title('Slope Distribution')
for i in range(len(V_DS[0])-1):
    plt.scatter(i, (V_DS[0][i+1]-V_DS[0][i])/(I_D[0][i+1]-I_D[0][i]))
fig1.set_dpi(150)
fig1.savefig('121.pdf')

y_intercepts = np.zeros(len(V_GS))
slope_fit = np.zeros(len(V_GS))
for i in range(len(V_GS)):
    slope, intercept, r_value, p_value, std_err =
    stats.linregress(V_DS[i][-2:], I_D[i][-2:])
    y_intercepts[i] = intercept
    slope_fit[i] = slope
print(slope_fit)
print(y_intercepts)

V_A = np.zeros(len(V_GS))
R_0 = np.zeros(len(V_GS))
fig1, ax1 = plt.subplots()
ax1.set_xlabel('Voltage (in V)')
ax1.set_ylabel('Current (in mA)')
ax1.set_ylim([-1.2,0])
ax1.set_title('$I_D$-$V_{DS}$ Characteristics of PMOS at different $V_{GS}$')
fig1.set_dpi(150)
intersect = 35
x = np.arange(-5,intersect,0.01)
for i in range(len(V_GS)):
    ax1.plot(x, 1000*(slope_fit[i]*x+y_intercepts[i]), '--o',
    markersize=0.01)
    ax1.plot(V_DS[i], 1000*I_D[i], '-o', markersize=0.01)
    V_A[i] = -y_intercepts[i]/slope_fit[i]
    R_0[i] = 1/slope_fit[i]
print(V_A)
print(np.mean(V_A))
print(R_0)
fig1.savefig('122.pdf')

```

```

data = pd.read_csv('E:\Program_Files\Spice64\EE236\Lab5\\211.txt', header =
None, skipinitialspace=True, delim_whitespace=True)
V_GS = data[0]
I_D = data[1]

fig1, ax1 = plt.subplots()
ax1.set_xlabel('Voltage $V_{GS}$ (in V)')
ax1.set_ylabel('Current $I_D$ (in mA)')
ax1.set_title('$I_D$-$V_{GS}$ Characteristics of PMOS at $V_{DS}$=-200mV$')
# ax1.legend(V_GS)
fig1.set_dpi(150)
slope, y_intercept, r_value, p_value, std_err = stats.linregress(V_GS[-2:],
1000*I_D[-2:])
ax1.plot(V_GS, slope*V_GS + y_intercept, '-o', markersize=0.01)
ax1.plot(V_GS, 1000*I_D, '-o', markersize=0.01)
print(y_intercept)
V_T = -y_intercept/slope
print("V_T =", V_T)
g_m = slope
print("g_m =", g_m) # in m mhos
fig1.savefig('21.pdf')

data = pd.read_csv('E:\Program_Files\Spice64\EE236\Lab5\\221.txt', header =
None, skipinitialspace=True, delim_whitespace=True)
V_GS = data[0]
I_D = data[1]
I_D_sqrt = [math.sqrt(i) for i in I_D]
fig1, ax1 = plt.subplots()
ax1.set_xlabel('Voltage $V_{GS}$ (in V)')
ax1.set_ylabel('Current $I_D$ (in mA)')
ax1.set_title('$I_D$-$V_{GS}$ Characteristics of PMOS at $V_{DS}$=-5V$')
# ax1.legend(V_GS)
fig1.set_dpi(150)
ax1.plot(V_GS, 1000*I_D, '-o', markersize=0.01)

fig2, ax2 = plt.subplots()
ax2.set_xlabel('Voltage $V_{GS}$ (in V)')
ax2.set_ylabel('$\sqrt{Current}$ $\sqrt{I_D}$ (in mA)')
ax2.set_title('$\sqrt{I_D}$-$V_{GS}$ Characteristics of PMOS at $V_{DS}$=-5V$')
slope, y_intercept, r_value, p_value, std_err = stats.linregress(V_GS[-2:],
(I_D_sqrt[-2:]))
ax2.plot(V_GS, slope*V_GS + y_intercept, '-o', markersize=0.01)
ax2.plot(V_GS, I_D_sqrt, '-o', markersize=0.01)
fig2.set_dpi(150)
V_T = -y_intercept/slope
print("V_T =", V_T)
K = 1000*2*slope**2

```

```

print("K =", K) # mA/V^2
# print(V_GS[300])
g_m = 1000*(I_D[301]-I_D[300]) / (V_GS[301]-V_GS[300])
print("g_m =", g_m) # in m mhos
fig1.savefig('221.pdf')
fig2.savefig('222.pdf')
# fig2.legend(["Characteristics", "Extrapolation"])

```

### 3.3.3 $I_D/V_{GS}$ characteristics of PMOS for different $V_{SB}$

```

V_SB = np.arange(0,-5,-1)

V_GS = []
I_D = []

fig1, ax1 = plt.subplots()
ax1.set_xlabel('Voltage $V_{GS}$ (in V)')
ax1.set_ylabel('Current $I_D$ (in mA)')
ax1.set_title('$I_D$-$V_{GS}$ Characteristics of PMOS at $V_{DS}$=-200mV$')

for i in range(len(V_SB)):
    data = pd.read_csv('E:\Program_Files\Spice64\EE236\Lab5\\31' + str(i+1)
        + '.txt', header = None, skipinitialspace=True, delim_whitespace=True)
    V_GS.append(data[0])
    I_D.append(data[1])
    ax1.plot(V_GS[i], 1000*I_D[i], '-o', markersize=0.01)
ax1.legend(V_SB)
fig1.set_dpi(150)
fig1.savefig('311.pdf')

y_intercepts = np.zeros(len(V_SB))
slope_fit = np.zeros(len(V_SB))
for i in range(len(V_SB)):
    slope, intercept, r_value, p_value, std_err =
        stats.linregress(V_GS[i][-2:], I_D[i][-2:])
    y_intercepts[i] = intercept
    slope_fit[i] = slope
print(slope_fit)
print(y_intercepts)

V_T = np.zeros(len(V_SB))
fig1, ax1 = plt.subplots()
ax1.set_xlabel('Voltage $V_{GS}$ (in V)')
ax1.set_xlim([-5,0])
ax1.set_ylabel('Current $I_D$ (in mA)')
ax1.set_ylim([-0.1,0.2])

```



```

ax1.set_title('$I_D-V_{GS}$ Characteristics of PMOS at $V_{DS}=-200mV$')
fig1.set_dpi(150)
intersect = 10
for i in range(len(V_SB)):
    x = np.arange(-y_intercepts[i]/slope_fit[i],intersect,0.01)
    ax1.plot(V_GS[i], 1000*I_D[i], '-o', markersize=0.01)
    V_T[i] = -y_intercepts[i]/slope_fit[i]
for i in range(len(V_SB)):
    ax1.plot(x, 1000*(slope_fit[i]*x+y_intercepts[i]), '--o',
            markersize=0.01)
print(V_T)
ax1.legend(V_SB)
fig1.savefig('312.pdf')

gamma = []
phi_s = 0.8
V_T0 = V_T[0]
for i in range(1,len(V_SB)):
    gamma.append((V_T[i] - V_T0)/(math.sqrt(phi_s-V_SB[i]) -
            math.sqrt(phi_s)))

gamma_avg = np.mean(gamma)
gamma_avg
V_Ta = np.zeros(len(V_SB))
for i in range(len(V_SB)):
    V_Ta[i] = V_T0 + gamma_avg*(math.sqrt(phi_s-V_SB[i]) - math.sqrt(phi_s))
fig1, ax1 = plt.subplots()
ax1.set_xlabel('Voltage $V_{T}$ (in V)')
ax1.set_ylabel('Voltage $V_{SB}$ (in V)')
ax1.plot(V_SB, V_T, '--om')
ax1.plot(V_SB, V_Ta, '--c')
fig1.set_dpi(150)
plt.legend(["Actual $V_T$", "Extrapolated $V_T$ using $\gamma_{avg}$"])
fig1.savefig('32.pdf')

```

## 4 Experiment completion status

Completed everything in Lab successfully.

## 5 Questions for reflection

The dependence of  $V_T$  on  $V_{SB}$  is similar to a square root graph which increases very slowly. As magnitude of  $V_T$  increases,  $V_{SB}$ 's magnitude decreases.

Please see my Design and Simulation Result sections for my other comments.

Overall, the lab was good.Thanks!