

Roll Number: 190070049


Name: Rathour Param Jitendrakumar

Course: Electronic Devices Lab

Course Code: EE236

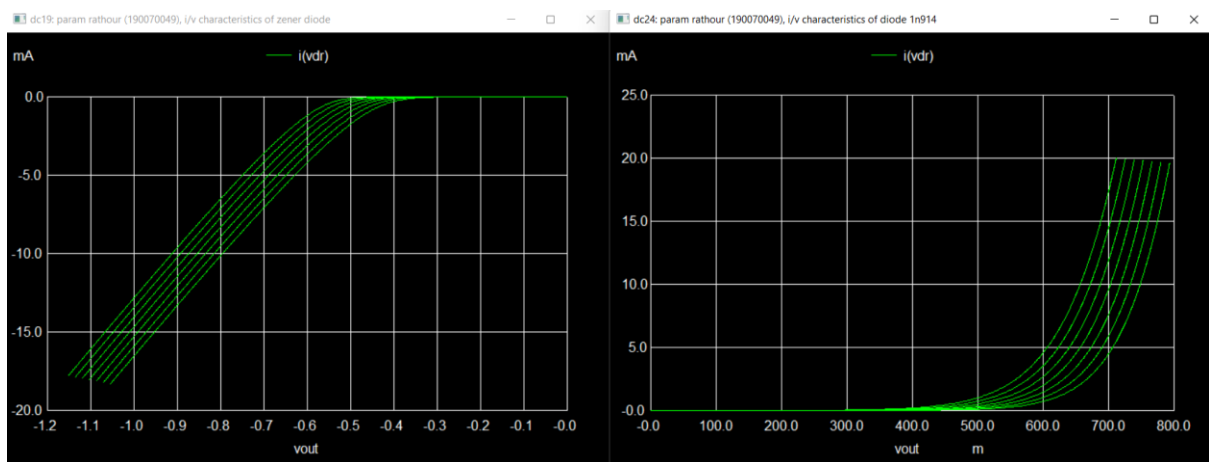Q1)


Zener (plot decreases as temperature increases) and 1N914 (plot goes leftwards)



For Zener,

```
In [47]: plt.plot(temp, [-0.566667, -0.544167, -0.520833, -0.499167, -0.48, -0.460833, -0.435833])
```
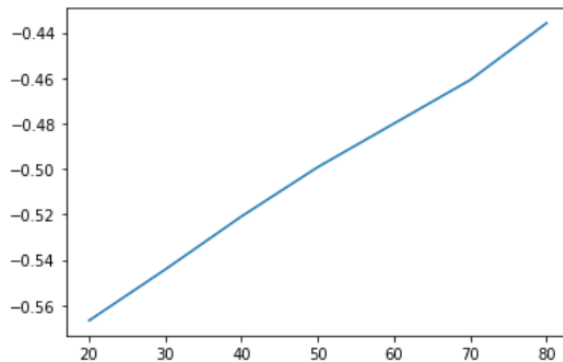
```
Out[47]: [ <matplotlib.lines.Line2D at 0x23dfb62b548>]
```



Tempcoeff in mV/C

```
In [50]: tempcoeff = (-0.566667 - (-0.435833)) / (20 - 80)
tempcoeff
```


```
Out[50]: 0.0021805666666666667
```

For 1N914

T tempcoeff in mV/C

```
In [54]: plt.plot(temp, [ 0.543889, 0.562778, 0.582222, 0.597222, 0.616111,0.635,0.655556])
tempcoeff = (0.543889-(0.655556))/(20-80)
tempcoeff
```

```
Out[54]: 0.001861116666666668
```

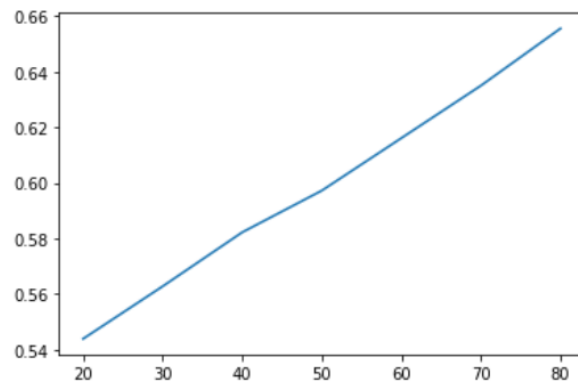

For both cases voltage across diode increases with temperature (positive TC)

Linear Plots

Q2)

In Voltage Regulator, Zener Diode maintains a steady voltage of 5.6V when  $R_S \geq 52.64\Omega$ ,

As max 1W power can flow in  $R_S$ , the maximum possible current flowing through it will be  $I_S = 1/5.6A$

when as breakdown voltage = 5.6V .

So,  $R_S = (V_S - V_Z)/(I_S) = (12 - 5.6)/(1/5.6) = 35.84\text{ohm}$

Negative terminal of Opamp is also 5.6V, So,

$R_1 = 144k\Omega$  and  $R_2 = 56k\Omega$  satisfy this, as the output required is 20V

