

# EE236: Experiment 5

## NMOS $I/V$ Characteristics and Applications

Param Rathour, 190070049  
Spring Semester, 2021-22

### Contents

<b>1</b>	<b>Overview of the experiment</b>	<b>3</b>
1.1	Aim of the experiment . . . . .	3
1.2	Methods . . . . .	3
1.2.1	NMOS . . . . .	3
1.2.2	CMOS Inverter . . . . .	3
<b>2</b>	<b>Design</b>	<b>4</b>
2.1	$I_D/V_{DS}$ Characteristics of NMOS . . . . .	4
2.2	$I_D/V_{GS}$ characteristics of NMOS for different $V_{DS}$ . . . . .	4
2.3	$I_D/V_{GS}$ characteristics of NMOS for different $V_{SB}$ . . . . .	5
2.4	CMOS Inverter Voltage Transfer Characteristics . . . . .	5
2.5	CMOS Inverter Transient Characteristics . . . . .	5
<b>3</b>	<b>Simulation results</b>	<b>6</b>
3.1	Plots . . . . .	6
3.1.1	$I_D/V_{DS}$ characteristics of NMOS for different $V_{GS}$ . . . . .	6
3.1.2	$I_D/V_{GS}$ characteristics of NMOS for different $V_{DS}$ . . . . .	7
3.1.3	$I_D/V_{GS}$ characteristics of NMOS for different $V_{SB}$ . . . . .	8
3.1.4	CMOS Inverter Voltage Transfer Characteristics . . . . .	9
3.1.5	CMOS Inverter Transient Characteristics . . . . .	10
3.2	NGSPICE Netlists . . . . .	11
3.2.1	$I_D/V_{DS}$ characteristics of NMOS for different $V_{GS}$ . . . . .	11
3.2.1.1	$V_{GS} = 2.5V$ . . . . .	11
3.2.1.2	$V_{GS} = 3V$ . . . . .	11
3.2.1.3	$V_{GS} = 3.5V$ . . . . .	11
3.2.1.4	$V_{GS} = 4V$ . . . . .	12
3.2.2	$I_D/V_{GS}$ characteristics of NMOS for different $V_{DS}$ . . . . .	12
3.2.2.1	$V_{DS} = -200mV$ . . . . .	12
3.2.2.2	$V_{DS} = -5V$ . . . . .	13
3.2.3	$I_D/V_{GS}$ characteristics of NMOS for different $V_{SB}$ . . . . .	13
3.2.3.1	$V_{SB} = 0$ . . . . .	13
3.2.3.2	$V_{SB} = 1V$ . . . . .	13
3.2.3.3	$V_{SB} = 2V$ . . . . .	14
3.2.3.4	$V_{SB} = 3V$ . . . . .	14

3.2.3.5	$V_{SB} = 4V$	15
3.2.4	CMOS Inverter: Voltage Transfer Characteristics dependence on $W_p, W_n$	15
3.2.4.1	$W_p/W_n = 60\mu m/30\mu m$	15
3.2.4.2	$W_p/W_n = 60\mu m/60\mu m$	16
3.2.4.3	$W_p/W_n = 30\mu m/60\mu m$	16
3.2.5	CMOS Inverter: Voltage Transfer Characteristics dependence on $V_{dd}$	17
3.2.5.1	$V_{dd} = 1.5V$	17
3.2.5.2	$V_{dd} = 2V$	17
3.2.5.3	$V_{dd} = 2.5V$	18
3.2.5.4	$V_{dd} = 3V$	18
3.2.5.5	$V_{dd} = 3.3V$	19
3.2.6	CMOS Inverter: Transient Characteristics dependence on $W_p, W_n$	19
3.2.6.1	$W_p/W_n = 60\mu m/30\mu m$	19
3.2.6.2	$W_p/W_n = 60\mu m/60\mu m$	20
3.2.6.3	$W_p/W_n = 30\mu m/60\mu m$	21
3.2.7	CMOS Inverter: Transient Characteristics dependence on $V_{dd}$	22
3.2.7.1	$V_{dd} = 2V$	22
3.2.7.2	$V_{dd} = 2.3V$	22
3.2.7.3	$V_{dd} = 2.6V$	23
3.2.7.4	$V_{dd} = 3V$	24
3.2.7.5	$V_{dd} = 3.3V$	25
3.3	Python Code for Plots and Calculations	25
3.3.1	$I_D/V_{DS}$ characteristics of NMOS for different $V_{GS}$	26
3.3.2	$I_D/V_{GS}$ characteristics of NMOS for different $V_{DS}$	27
3.3.3	$I_D/V_{GS}$ characteristics of NMOS for different $V_{SB}$	29
3.4	CMOS Inverter Voltage Transfer Characteristics	30
3.4.1	CMOS Inverter Transient Characteristics	33
<b>4</b>	<b>Experiment completion status</b>	<b>33</b>
<b>5</b>	<b>Questions for reflection</b>	<b>33</b>

# 1 Overview of the experiment

This report contains my approach to the experiment, the circuit's design with the relevant simulation code and output plots.

## 1.1 Aim of the experiment

- To plot and understand  $I_D/V_{DS}$  characteristics of NMOS at different  $V_{GS}$  and calculate  $r_{DS}$  (resistance linear region),  $r_0$  (resistance saturation region) and  $V_A$  (early voltage) considering channel length modulation.
- To plot and understand  $I_D/V_{GS}$  characteristics of NMOS in different regions and obtain the parameters  $V_T$ ,  $g_m$  and  $K$  (in  $mA/V^2$ )
- To plot and understand the effect of Body Bias on  $I_D/V_{GS}$  characteristics of NMOS and calculate  $\gamma$  (body effect coefficient)
- To plot and understand voltage transfer characteristics and transient characteristics of CMOS inverter

## 1.2 Methods

### 1.2.1 NMOS

First,  $I_D/V_{DS}$  characteristics of NMOS at different  $V_{GS}$  was plotted and the parameters were calculated & compared.

Then,  $I_D/V_{GS}$  characteristics of NMOS at was plotted in different regions by changing  $V_{DS}$  and the parameters were calculated.

Lastly,  $I_D/V_{GS}$  characteristics of NMOS at was plotted for different body voltage and behaviour of  $V_T$  verses  $V_{SB}$  was observed which was used to calculate body effect coefficient.

All figures & parameters were calculated using Python by exporting the NGSPICE vectors.

### 1.2.2 CMOS Inverter

First, Voltage Transfer Characteristics ( $V_{out}$  vs  $V_{in}$ ) was plotted for

$W_p/W_n = 60um/30um, 60um/60um, 30um/60um$  and switching threshold was calculated respectively.

Then, Voltage Transfer Characteristics ( $V_{out}$  vs  $V_{in}$ ) was plotted for various  $V_{dd} = 1.5V, 2V, 2.5V, 3V, 3.3V$  and the VTC curves were observed.

All figures & parameters were calculated using Python by exporting the NGSPICE vectors.


Then, Rise ( $t_r$ ), Fall ( $t_f$ ), Propagation ( $t_p$ ) delays were calculated using Transient Characteristics for  $W_p/W_n = 60um/30um, 60um/60um, 30um/60um$ .

Lastly, Propagation ( $t_p$ ) delays were calculated using Transient Characteristics for various  $V_{dd} = 2V, 2.3V, 2.6V, 3V, 3.3V$ .


All parameters were calculated using NGSPICE and figures using Python.
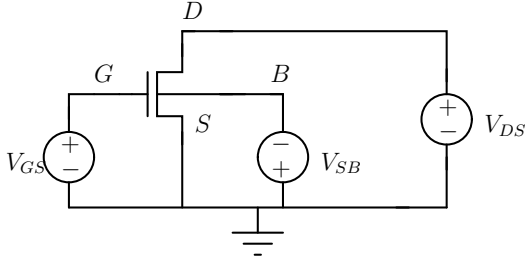
## 2 Design

The common circuits designed for all parts are shown below



(a) Circuit for I/V measurement of NMOS

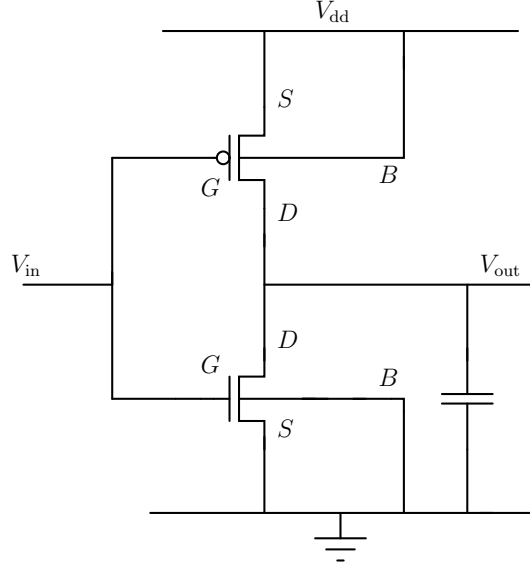

(b) Circuit for characteristics of CMOS inverter

### 2.1 $I_D/V_{DS}$ Characteristics of NMOS

For the first part the Voltage  $V_{GS}$  was varied from  $2.5V$  to  $4V$  in steps of  $0.5V$ .

For each  $V_{GS}$ ,  $V_{DS}$  was varied from  $0$  to  $5V$

As in linear region slope  $I_D/V_{DS}$  is maximum  $\rightarrow r_{DS} = \frac{1}{\text{maximum slope}}$

Similarly in saturation region slope  $I_D/V_{DS}$  is minimum  $\rightarrow r_0 = \frac{1}{\text{minimum slope}}$

Early voltage can be calculated by taking the mean of the  $x$ -intercepts of the extrapolated lines from saturation regions.

$$x - \text{intercept} = \frac{-(y - \text{intercept})}{\text{slope}}$$

and slope,  $y$ -intercepts were calculated using Python's **Scipy** package This graph is a straight line in some range of  $I, V$ . Also,  $I_L = 0$  for Dark characteristics.

We can calculate its slope to get  $\eta$  and  $y$ -intercept by interpolating that straight line.

### 2.2 $I_D/V_{GS}$ characteristics of NMOS for different $V_{DS}$

Again, the above circuit was used (Figure 1a),  $V_{GS}$  was varied from  $0$  to  $5V$

$$I_D = \frac{1}{2}K(2(V_{GS} - V_T)V_{DS} - (V_{DS})^2)$$

In linear region,  $(V_{DS})^2$  can be ignored (as  $V_{DS} = 200mV$ ) to give

$$I_D = K(V_{GS} - V_T)V_{DS}$$

So  $V_T = -\underbrace{(y - \text{intercept})}_{-K \cdot V_T \cdot V_{DS}} / \underbrace{\text{slope}}_{K \cdot V_{DS}}$  and  $g_m = \frac{\partial I_D}{\partial V_{GS}} = \frac{I_D}{V_{GS}}$  (as the plot is linear)

In saturation region, as  $V_{DS} = 5V \leq (V_{GS} - V_T)$ ,  $I_D$  depends only on  $(V_{GS} - V_T)$  (ideally)

$$I_D = \frac{1}{2} K (V_{GS} - V_T)^2$$

$$\sqrt{I_D} = \frac{1}{\sqrt{2}} \sqrt{K} (V_{GS} - V_T)$$

So from the  $\sqrt{I_D}/V_{GS}$  characteristics,  $K = 2 \cdot \text{slope}^2$  (in  $A/V^2$ ) =  $1000 \cdot 2 \cdot \text{slope}^2$  (in  $mA/V^2$ )

$$V_T = -\underbrace{(y - \text{intercept})}_{-\frac{1}{\sqrt{2}} \sqrt{K} \cdot V_T} / \underbrace{\text{slope}}_{\frac{1}{\sqrt{2}} \sqrt{K}}$$

and  $g_m = \frac{\partial I_D}{\partial V_{GS}}$  will be different for different  $V_{GS}$  (as the plot is quadratic)

Say,  $V_{GS} = 3V$ , then at that point,  $g_m = \frac{I_D}{V_{GS}} \mathcal{U}$

## 2.3 $I_D/V_{GS}$ characteristics of NMOS for different $V_{SB}$

Again, the same circuit ((Figure 1a)) was used.

With  $V_{SB}$  varying from 0 to 4V in steps of 1V.  $V_{DS} = 200mV$

To calculate  $V_T$ , again we extrapolate the lines and get the  $x - \text{intercept}$ .

Then  $\gamma$  was calculated for each  $V_T$  and  $V_{SB}$  as shown below (average of all  $\gamma$  was taken)

$$V_T = V_{T0} + \gamma(\sqrt{\varphi_s + V_{SB}} - \sqrt{\varphi_s}) \quad (\text{where } \varphi_s = 0.8V)$$

## 2.4 CMOS Inverter Voltage Transfer Characteristics

The circuit used is shown in (Figure 1b) with MOSFETs instantiated using the given templates

$V_{dd} = 3.3V$  and Load capacitance was taken as  $0.05pF$

$V_{in}$  was varied from 0 to 3.3V to obtain Voltage Transfer Characteristics ( $V_{out}$  vs  $V_{in}$ )

The switching threshold was calculated in 2 ways, First, when in the simulation  $V_{out}$  and  $V_{in}$  were closest.

Second, when the slope of  $V_{out}$  vs  $V_{in}$  was maximum.

Average of both  $V_{out}$  and  $V_{in}$  at such point was taken as the answer.

Note that both approach yielded same answers.

As ideally at such point  $V_{out} = V_{in}$  and slope is infinity (due to symmetry).

## 2.5 CMOS Inverter Transient Characteristics

Here, again the same circuit (Figure 1b) was used. Transient Analysis was done and the parameters  $t_r, t_f, t_{pr}, t_{pf}, t_p$  were calculated using definition given in handout.

For the first task,  $W_p/W_n$  was varied from  $60um/30um, 60um/60um, 30um/60um$  and

For the second task  $V_{dd}$  was varied from 2V, 2.3V, 2.6V, 3V, 3.3V


### 3 Simulation results

#### 3.1 Plots


##### 3.1.1 $I_D/V_{DS}$ characteristics of NMOS for different $V_{GS}$

$V_{GS}$ (in V)	$R_{DS}$ (in $\Omega$ )	$V_A$ (in V)	$R_0$ (in $\Omega$ )
2.5	1237.6478888513582	34.48275886	47301.45215462
3	968.0078253752603	34.48190104	28970.39225912
3.5	794.8400573159166	34.48198702	19547.66698594
4	674.2269987459377	34.48234203	14073.01077994


Table 1: Parameter Values obtained from the characteristics

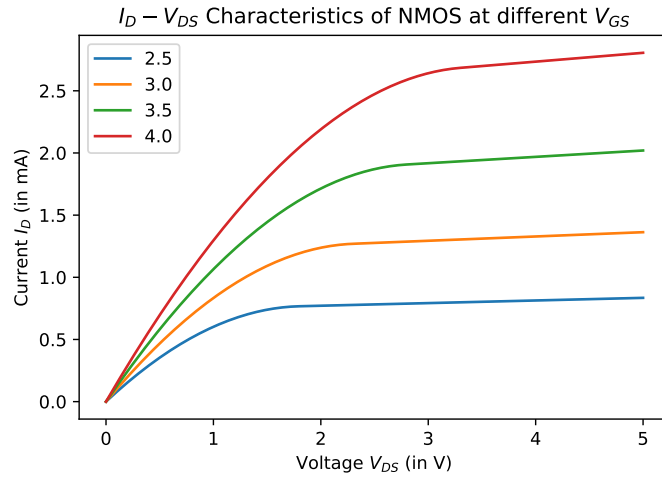

(a) Different  $V_{GS}$

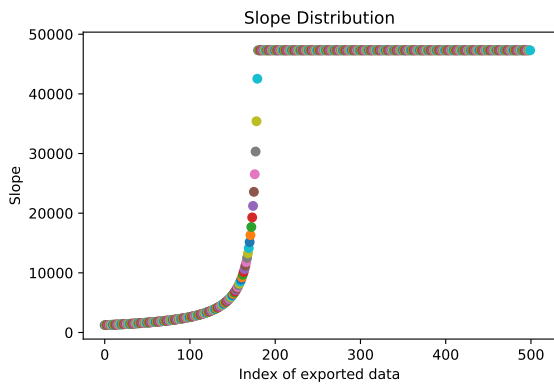

(b) Slope Distribution

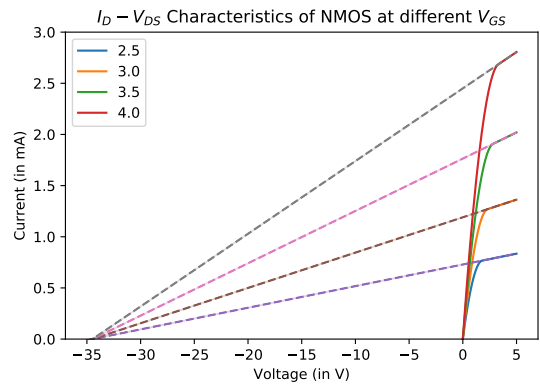

(c) Characteristics with the Extrapolated Lines

Figure 2:  $I_D/V_{DS}$  characteristics of NMOS

In Figure 2, as magnitude of  $V_{GS}$  increases, magnitude of  $I_D$  increases.

All extrapolated lines meet at  $V_A = 34.48224723629818$   
 Also, both  $R_{DS}$  and  $R_0$  decreases with the increase of  $V_{GS}$ .

### 3.1.2 $I_D/V_{GS}$ characteristics of NMOS for different $V_{DS}$

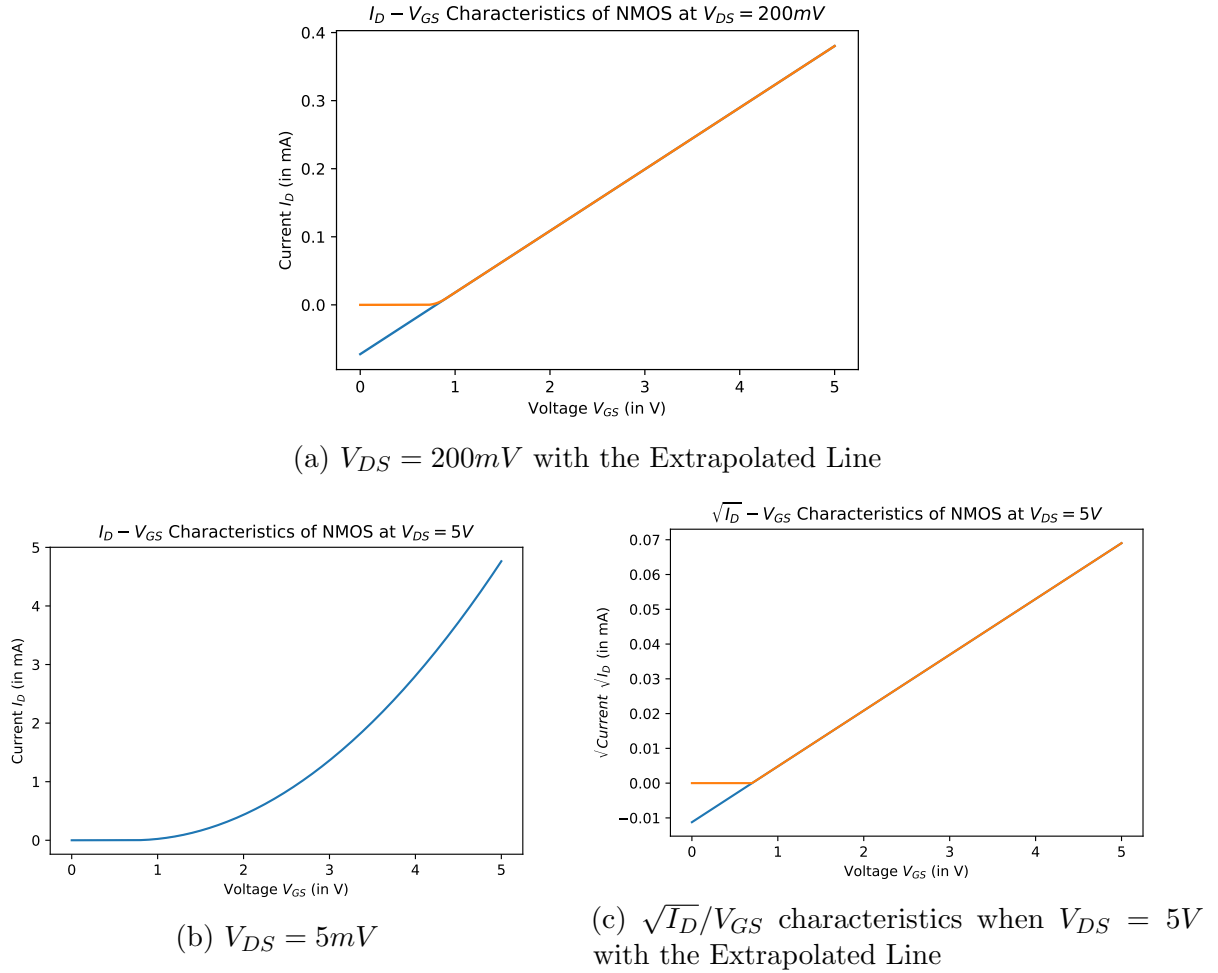


Figure 3:  $I_D/V_{GS}$  characteristics of NMOS

In Figure 3a), as magnitude of  $V_{GS}$  increases (neglecting the small  $V_{GS}$  values as NMOS is saturated), magnitude of  $I_D$  increases linearly giving

$$V_T = 0.8V \text{ and } g_m = 0.090522m\mathcal{U}$$

In Figure 3b), as magnitude of  $V_{GS}$  increases (neglecting the small  $V_{GS}$  values as NMOS is not saturated), magnitude of  $I_D$  increases quadratically giving

$$V_T = 0.7V, g_m = 1.187651m\mathcal{U} \text{ (at } V_{GS} = 3V) \text{ and } K = 0.5152501154659527mA/V^2$$

$V_T$  is different in both cases, because of approximations in the current ( $I_D$ ) equation and neglect of channel length modulation.

### 3.1.3 $I_D/V_{GS}$ characteristics of NMOS for different $V_{SB}$

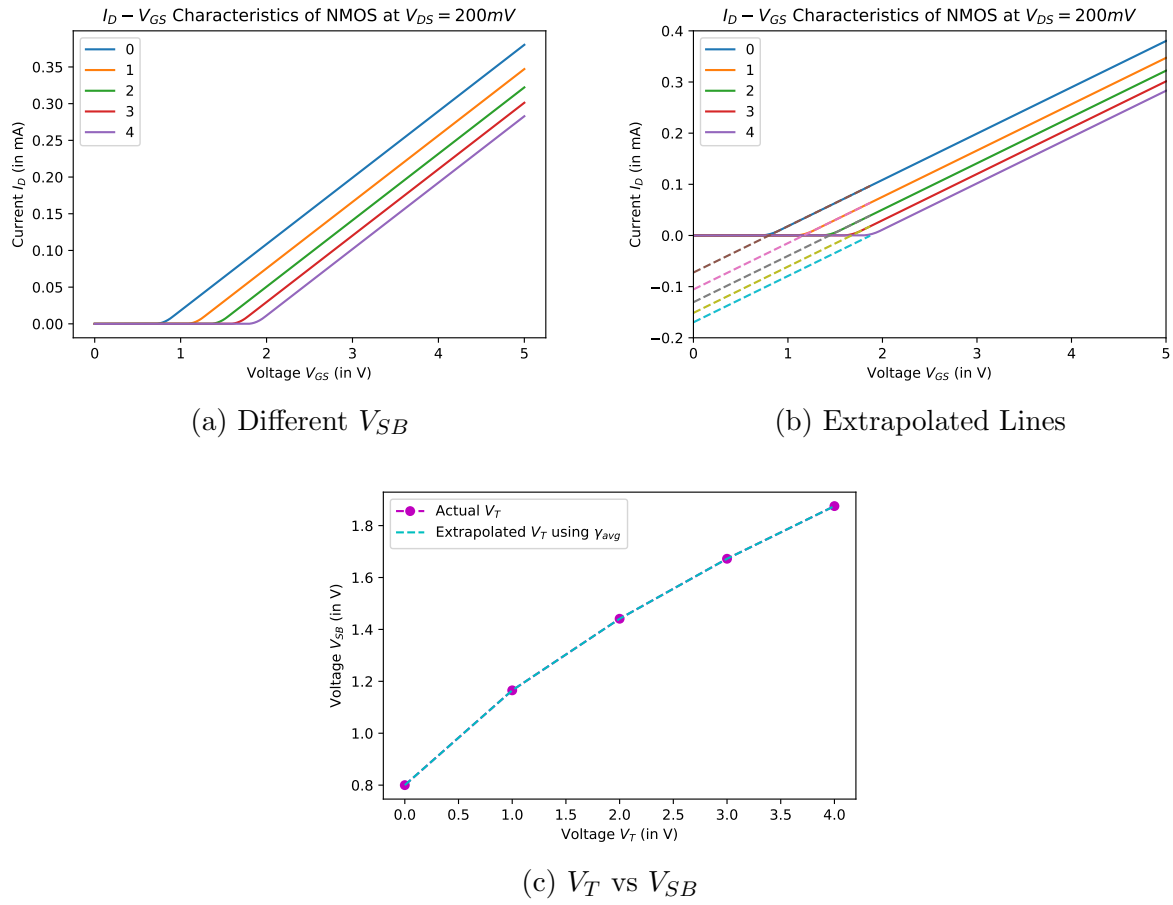


Figure 4:  $I_D/V_{GS}$  characteristics of NMOS

In Figure 4, as magnitude of  $V_{SB}$  increases, magnitude of  $I_D$  reduces giving  $V_T = 0.8V, 1.16526333V, 1.44111701V, 1.67223466V, 1.87517436V$  for  $V_{SB} = 0V, 1V, 2V, 3V, 4V$  respectively.

From these values, we get  $\gamma = 0.85\sqrt{V}$  and it fits the original curve very well.

The dependence of  $V_T$  on  $V_{SB}$  is similar to a square root graph which increases very slowly. As magnitude of  $V_T$  increases,  $V_{SB}$ 's magnitude increases but the rate of increase decreases.



### 3.1.4 CMOS Inverter Voltage Transfer Characteristics

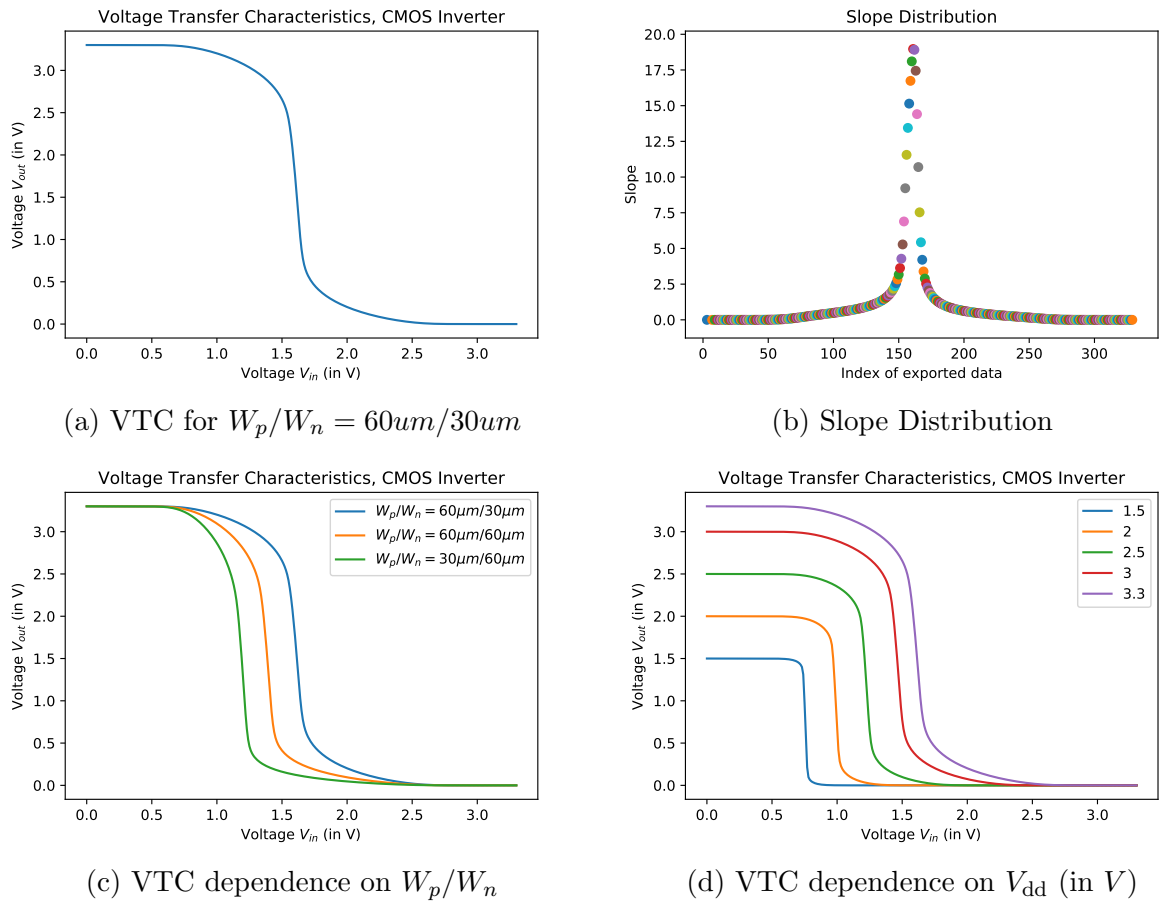


Figure 5: CMOS Inverter Voltage Transfer Characteristics

$W_p/W_n$ (in $\mu\text{m}/\mu\text{m}$ )	Switching Threshold (in V)
60/30 $\mu\text{m}$	1.596188005
60 $\mu\text{m}/60\mu\text{m}$	1.417962135
30 $\mu\text{m}/60\mu\text{m}$	1.244664655

Table 2: Parameter Values obtained from the characteristics

From the Figure 5,

As  $W_p/W_n$  decreases, the high slope (vertical) part of VTCs shift leftwards and the switching threshold decreases.

As  $V_{dd}$  increases, the high slope (vertical) part of VTCs shift rightwards and the maximum  $V_{out}$  value increases.

### 3.1.5 CMOS Inverter Transient Characteristics

$W_p/W_n$ (in $um/um$ )	$t_r$ (in s)	$t_f$ (in s)	$t_{pr}$ (in s)	$t_{pf}$ (in s)	$t_p$ (in s)
60/30	4.665700e-11	3.676000e-11	3.407600e-11	3.523700e-11	3.465650e-11
60/60	5.675300e-11	2.373900e-11	4.213600e-11	2.368700e-11	3.291150e-11
30/60	8.996600e-11	1.992900e-11	6.511800e-11	1.933100e-11	4.222450e-11

Table 3: Delay parameter Values obtained from the characteristics

As  $W_p/W_n$  decreases,  $t_r, t_{pr}$  increases,  $t_f, t_{pf}$  decreases and  $t_p$  first increases then decreases.

This shows that ‘rise’ delays increase and ‘fall’ delays decrease with decrease in  $W_p/W_n$ .

Propagation delay  $t_p$  which is an average of ‘rise’ and ‘fall’ delay will increase/decrease depending on which factor got affected more.

Next, for  $W_p/W_n = 60um/30um$ , the variation of propagation delays with  $V_{dd}$  is shown

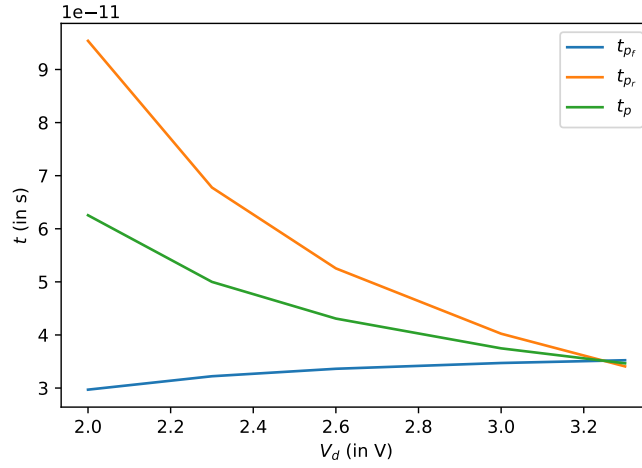


Figure 6: Variation of Propagation Delays with  $V_{dd}$   
CMOS Inverter Transient Characteristics

As shown in Figure 6,

The rise propagation delay decreases with increase in  $V_{dd}$

The fall propagation delay increase with increase in  $V_{dd}$

The ‘rise’ delay factor got affected more than ‘fall’ delay factor.

Hence, propagation delay decreases with increase in  $V_{dd}$ .

## 3.2 NGSPICE Netlists

### 3.2.1 $I_D/V_{DS}$ characteristics of NMOS for different $V_{GS}$

#### 3.2.1.1 $V_{GS} = 2.5V$

```
Param Rathour (190070049), I_D - V_DS Characteristics of NMOS at V_GS = 2.5V
.include ALD1105N.txt           ; Includes NMOS Model
M1 d g gnd gnd ALD1105N
VD mid gnd 0
Vdummy d mid 0
VG g gnd 2.5
.dc VD 0 5 0.01                ; DC Analysis
.control
run
let I_D = -I(Vdummy)
let V_DS = V(d)
plot I_D vs V_DS
wrdata 111.txt I_D vs V_DS
.endc
.end
```

#### 3.2.1.2 $V_{GS} = 3V$

```
Param Rathour (190070049), I_D - V_DS Characteristics of NMOS at V_GS = 3V
.include ALD1105N.txt           ; Includes NMOS Model
M1 d g gnd gnd ALD1105N
VD mid gnd 0
Vdummy d mid 0
VG g gnd 3
.dc VD 0 5 0.01                ; DC Analysis
.control
run
let I_D = -I(Vdummy)
let V_DS = V(d)
plot I_D vs V_DS
wrdata 112.txt I_D vs V_DS
.endc
.end
```

#### 3.2.1.3 $V_{GS} = 3.5V$

```
Param Rathour (190070049), I_D - V_DS Characteristics of NMOS at V_GS = 3.5V
.include ALD1105N.txt           ; Includes NMOS Model
M1 d g gnd gnd ALD1105N
VD mid gnd 0
```

```

Vdummy d mid 0
VG g gnd 3.5
.dc VD 0 5 0.01          ; DC Analysis
.control
run
let I_D = -I(Vdummy)
let V_DS = V(d)
plot I_D vs V_DS
wrdata 113.txt I_D vs V_DS
.endc
.end

```

#### 3.2.1.4 $V_{GS} = 4V$

```

Param Rathour (190070049), I_D - V_DS Characteristics of NMOS at V_GS = 4V
.include ALD1105N.txt      ; Includes NMOS Model
M1 d g gnd gnd ALD1105N
VD mid gnd 0
Vdummy d mid 0
VG g gnd 4
.dc VD 0 5 0.01          ; DC Analysis
.control
run
let I_D = -I(Vdummy)
let V_DS = V(d)
plot I_D vs V_DS
wrdata 114.txt I_D vs V_DS
.endc
.end

```

### 3.2.2 $I_D/V_{GS}$ characteristics of NMOS for different $V_{DS}$

#### 3.2.2.1 $V_{DS} = -200mV$

```

Param Rathour (190070049), I_D - V_GS Characteristics of NMOS at V_DS = 200mV
.include ALD1105N.txt      ; Includes NMOS Model
M1 d g gnd gnd ALD1105N
VD mid gnd 200m
Vdummy d mid 0
VG g gnd 0
.dc VG 0 5 0.01          ; DC Analysis
.control
run
let I_D = -I(Vdummy)
let V_GS = V(g)
plot I_D vs V_GS

```

```
wrdata 211.txt I_D vs V_GS
.endc
.end
```

### 3.2.2.2 $V_{DS} = -5V$

```
Param Rathour (190070049), I_D - V_GS Characteristics of NMOS at V_DS = 5V
.include ALD1105N.txt           ; Includes NMOS Model
M1 d g gnd gnd ALD1105N
VD mid gnd 5
Vdummy d mid 0
VG g gnd 0
.dc VG 0 5 0.01                ; DC Analysis
.control
run
let I_D = -I(Vdummy)
let V_GS = V(g)
plot I_D vs V_GS
wrdata 221.txt I_D vs V_GS
.endc
.end
```

### 3.2.3 $I_D/V_{GS}$ characteristics of NMOS for different $V_{SB}$

#### 3.2.3.1 $V_{SB} = 0$

```
Param Rathour (190070049), Effect of Body Bias
.include ALD1105N.txt           ; Includes NMOS Model
M1 d g gnd b ALD1105N
VD mid gnd 200m
Vdummy d mid 0
VG g gnd 0
VB b gnd 0
.dc VG 0 5 0.01                ; DC Analysis
.control
run
let I_D = -I(Vdummy)
let V_GS = V(g)
plot I_D vs V_GS
wrdata 311.txt I_D vs V_GS
.endc
.end
```

#### 3.2.3.2 $V_{SB} = 1V$

```

Param Rathour (190070049), Effect of Body Bias
.include ALD1105N.txt           ; Includes NMOS Model
M1 d g gnd b ALD1105N
VD mid gnd 200m
Vdummy d mid 0
VG g gnd 0
VB b gnd -1
.dc VG 0 5 0.01                ; DC Analysis
.control
run
let I_D = -I(Vdummy)
let V_GS = V(g)
plot I_D vs V_GS
wrdata 312.txt I_D vs V_GS
.endc
.end

```

### 3.2.3.3 $V_{SB} = 2V$

```

Param Rathour (190070049), Effect of Body Bias
.include ALD1105N.txt           ; Includes NMOS Model
M1 d g gnd b ALD1105N
VD mid gnd 200m
Vdummy d mid 0
VG g gnd 0
VB b gnd -2
.dc VG 0 5 0.01                ; DC Analysis
.control
run
let I_D = -I(Vdummy)
let V_GS = V(g)
plot I_D vs V_GS
wrdata 313.txt I_D vs V_GS
.endc
.end

```

### 3.2.3.4 $V_{SB} = 3V$

```

Param Rathour (190070049), Effect of Body Bias
.include ALD1105N.txt           ; Includes NMOS Model
M1 d g gnd b ALD1105N
VD mid gnd 200m
Vdummy d mid 0
VG g gnd 0

```

```

VB b gnd -3
.dc VG 0 5 0.01          ; DC Analysis
.control
run
let I_D = -I(Vdummy)
let V_GS = V(g)
plot I_D vs V_GS
wrdata 314.txt I_D vs V_GS
.endc
.end

```

### 3.2.3.5 $V_{SB} = 4V$

```

Param Rathour (190070049), Effect of Body Bias
.include ALD1105N.txt      ; Includes NMOS Model
M1 d g gnd b ALD1105N
VD mid gnd 200m
Vdummy d mid 0
VG g gnd 0
VB b gnd -4
.dc VG 0 5 0.01          ; DC Analysis
.control
run
let I_D = -I(Vdummy)
let V_GS = V(g)
plot I_D vs V_GS
wrdata 315.txt I_D vs V_GS
.endc
.end

```

## 3.2.4 CMOS Inverter: Voltage Transfer Characteristics dependence on $W_p$ , $W_n$

### 3.2.4.1 $W_p/W_n = 60\mu m/30\mu m$

```

Param Rathour (190070049), CMOS Inverter
.include CMOS.txt          ; Includes NMOS Model
.param Wn = {30u} Wp = {60u} Len = {0.4u}
* M drain gate source body cmos
Mn out in gnd gnd cmosn L=Len W=Wn AS={2*Wn*Len} PS={2*Wn+4*Len}
  AD={2*Wn*Len} PD={2*Wn+4*Len}
Mp out in Vdd Vdd cmosp L=Len W=Wp AS={2*Wp*Len} PS={2*Wp+4*Len}
  AD={2*Wp*Len} PD={2*Wp+4*Len}
C1 out gnd 0.05p
Vdd Vdd gnd 3.3
Vin in gnd 0
.dc Vin 0 3.3 0.01

```

```

.control
run
plot V(out) vs V(in)
wrdata 411.txt V(out) vs V(in)
.endc
.end

```

### 3.2.4.2 $W_p/W_n = 60\mu m/60\mu m$

```

Param Rathour (190070049), CMOS Inverter
.include CMOS.txt           ; Includes NMOS Model
.param Wn = {60u} Wp = {60u} Len = {0.4u}
* M drain gate source body cmos
Mn out in gnd gnd cmosn L=Len W=Wn AS={2*Wn*Len} PS={2*Wn+4*Len}
    AD={2*Wn*Len} PD={2*Wn+4*Len}
Mp out in Vdd Vdd cmosp L=Len W=Wp AS={2*Wp*Len} PS={2*Wp+4*Len}
    AD={2*Wp*Len} PD={2*Wp+4*Len}
C1 out gnd 0.05p
Vdd Vdd gnd 3.3
Vin in gnd 0
.dc Vin 0 3.3 0.01
.control
run
plot V(out) vs V(in)
wrdata 412.txt V(out) vs V(in)
.endc
.end

```

### 3.2.4.3 $W_p/W_n = 30\mu m/60\mu m$

```

Param Rathour (190070049), CMOS Inverter
.include CMOS.txt           ; Includes NMOS Model
.param Wn = {60u} Wp = {30u} Len = {0.4u}
* M drain gate source body cmos
Mn out in gnd gnd cmosn L=Len W=Wn AS={2*Wn*Len} PS={2*Wn+4*Len}
    AD={2*Wn*Len} PD={2*Wn+4*Len}
Mp out in Vdd Vdd cmosp L=Len W=Wp AS={2*Wp*Len} PS={2*Wp+4*Len}
    AD={2*Wp*Len} PD={2*Wp+4*Len}
C1 out gnd 0.05p
Vdd Vdd gnd 3.3
Vin in gnd 0
.dc Vin 0 3.3 0.01
.control
run
plot V(out) vs V(in)

```



```
wrdata 413.txt V(out) vs V(in)
.endc
.end
```

### 3.2.5 CMOS Inverter: Voltage Transfer Characteristics dependence on $V_{dd}$

#### 3.2.5.1 $V_{dd} = 1.5V$

```
Param Rathour (190070049), CMOS Inverter
.include CMOS.txt ; Includes NMOS Model
.param Wn = {30u} Wp = {60u} Len = {0.4u}
* M drain gate source body cmos
Mn out in gnd gnd cmosn L=Len W=Wn AS={2*Wn*Len} PS={2*Wn+4*Len}
    AD={2*Wn*Len} PD={2*Wn+4*Len}
Mp out in Vdd Vdd cmosp L=Len W=Wp AS={2*Wp*Len} PS={2*Wp+4*Len}
    AD={2*Wp*Len} PD={2*Wp+4*Len}
C1 out gnd 0.05p
Vdd Vdd gnd 1.5
Vin in gnd 0
.dc Vin 0 3.3 0.01
.control
run
plot V(out) vs V(in)
wrdata 421.txt V(out) vs V(in)
.endc
.end
```

#### 3.2.5.2 $V_{dd} = 2V$

```
Param Rathour (190070049), CMOS Inverter
.include CMOS.txt ; Includes NMOS Model
.param Wn = {30u} Wp = {60u} Len = {0.4u}
* M drain gate source body cmos
Mn out in gnd gnd cmosn L=Len W=Wn AS={2*Wn*Len} PS={2*Wn+4*Len}
    AD={2*Wn*Len} PD={2*Wn+4*Len}
Mp out in Vdd Vdd cmosp L=Len W=Wp AS={2*Wp*Len} PS={2*Wp+4*Len}
    AD={2*Wp*Len} PD={2*Wp+4*Len}
C1 out gnd 0.05p
Vdd Vdd gnd 2
Vin in gnd 0
.dc Vin 0 3.3 0.01
.control
run
plot V(out) vs V(in)
wrdata 422.txt V(out) vs V(in)
.endc
```

```
.end
```

### 3.2.5.3 $V_{dd} = 2.5V$

```
Param Rathour (190070049), CMOS Inverter
.include CMOS.txt           ; Includes NMOS Model
.param Wn = {30u} Wp = {60u} Len = {0.4u}
* M drain gate source body cmos
Mn out in gnd gnd cmosn L=Len W=Wn AS={2*Wn*Len} PS={2*Wn+4*Len}
    AD={2*Wn*Len} PD={2*Wn+4*Len}
Mp out in Vdd Vdd cmosp L=Len W=Wp AS={2*Wp*Len} PS={2*Wp+4*Len}
    AD={2*Wp*Len} PD={2*Wp+4*Len}
C1 out gnd 0.05p
Vdd Vdd gnd 2.5
Vin in gnd 0
.dc Vin 0 3.3 0.01
.control
run
plot V(out) vs V(in)
wrdata 423.txt V(out) vs V(in)
.endc
.end
```

### 3.2.5.4 $V_{dd} = 3V$

```
Param Rathour (190070049), CMOS Inverter
.include CMOS.txt           ; Includes NMOS Model
.param Wn = {30u} Wp = {60u} Len = {0.4u}
* M drain gate source body cmos
Mn out in gnd gnd cmosn L=Len W=Wn AS={2*Wn*Len} PS={2*Wn+4*Len}
    AD={2*Wn*Len} PD={2*Wn+4*Len}
Mp out in Vdd Vdd cmosp L=Len W=Wp AS={2*Wp*Len} PS={2*Wp+4*Len}
    AD={2*Wp*Len} PD={2*Wp+4*Len}
C1 out gnd 0.05p
Vdd Vdd gnd 3
Vin in gnd 0
.dc Vin 0 3.3 0.01
.control
run
plot V(out) vs V(in)
wrdata 424.txt V(out) vs V(in)
.endc
.end
```

### 3.2.5.5 $V_{dd} = 3.3V$

```
Param Rathour (190070049), CMOS Inverter
.include CMOS.txt           ; Includes NMOS Model
.param Wn = {30u} Wp = {60u} Len = {0.4u}
* M drain gate source body cmos
Mn out in gnd gnd cmosn L=Len W=Wn AS={2*Wn*Len} PS={2*Wn+4*Len}
    AD={2*Wn*Len} PD={2*Wn+4*Len}
Mp out in Vdd Vdd cmosp L=Len W=Wp AS={2*Wp*Len} PS={2*Wp+4*Len}
    AD={2*Wp*Len} PD={2*Wp+4*Len}
C1 out gnd 0.05p
Vdd Vdd gnd 3.3
Vin in gnd 0
.dc Vin 0 3.3 0.01
.control
run
plot V(out) vs V(in)
wrdata 425.txt V(out) vs V(in)
.endc
.end
```

### 3.2.6 CMOS Inverter: Transient Characteristics dependence on $W_p$ , $W_n$

#### 3.2.6.1 $W_p/W_n = 60\mu m/30\mu m$

```
Param Rathour (190070049), CMOS Inverter
.include CMOS.txt           ; Includes NMOS Model
.param Wn = {30u} Wp = {60u} Len = {0.4u}
.param Vd = 3.3
* M drain gate source body cmos
Mn out in gnd gnd cmosn L=Len W=Wn AS={2*Wn*Len} PS={2*Wn+4*Len}
    AD={2*Wn*Len} PD={2*Wn+4*Len}
Mp out in Vdd Vdd cmosp L=Len W=Wp AS={2*Wp*Len} PS={2*Wp+4*Len}
    AD={2*Wp*Len} PD={2*Wp+4*Len}
C1 out gnd 0.05p
Vdd Vdd gnd Vd
Vin in gnd pulse(0 Vd 0 20p 20p 4n 8n)
* .dc Vin 0 Vd 0.01
.tran 1p 30n
.control
let Vddd = 3.3
run
let l = {Vddd*0.1}
let h = {Vddd*0.9}
let mid = {Vddd*0.5}
meas tran tr1 WHEN V(out) = 1 CROSS = 2
```

```

meas tran tr2 WHEN V(out) = h CROSS = 2
let tr = tr2-tr1
meas tran tf1 WHEN V(out) = l CROSS = 3
meas tran tf2 WHEN V(out) = h CROSS = 3
let tf = tf1-tf2
meas tran tpr1 WHEN V(in) = mid CROSS = 2
meas tran tpr2 WHEN V(out) = mid CROSS = 2
let tpr = tpr2-tpr1
meas tran tpf1 WHEN V(in) = mid CROSS = 3
meas tran tpf2 WHEN V(out) = mid CROSS = 3
let tpf = tpf2-tpf1
let tp = (tpr + tpf)/2
print tr tf tpr tpf tp
plot V(out) V(in)
wrdata 431.txt V(out)
.endc
.end

```

### 3.2.6.2 $W_p/W_n = 60\mu m/60\mu m$

```

Param Rathour (190070049), CMOS Inverter
.include CMOS.txt ; Includes NMOS Model
.param Wn = {60u} Wp = {60u} Len = {0.4u}
.param Vd = 3.3
* M drain gate source body cmos
Mn out in gnd gnd cmosn L=Len W=Wn AS={2*Wn*Len} PS={2*Wn+4*Len}
    AD={2*Wn*Len} PD={2*Wn+4*Len}
Mp out in Vdd Vdd cmosp L=Len W=Wp AS={2*Wp*Len} PS={2*Wp+4*Len}
    AD={2*Wp*Len} PD={2*Wp+4*Len}
C1 out gnd 0.05p
Vdd Vdd gnd Vd
Vin in gnd pulse(0 Vd 0 20p 20p 4n 8n)
* .dc Vin 0 Vd 0.01
.tran 1p 30n
.control
let Vddd = 3.3
run
let l = {Vddd*0.1}
let h = {Vddd*0.9}
let mid = {Vddd*0.5}
meas tran tr1 WHEN V(out) = l CROSS = 2
meas tran tr2 WHEN V(out) = h CROSS = 2
let tr = tr2-tr1
meas tran tf1 WHEN V(out) = l CROSS = 3
meas tran tf2 WHEN V(out) = h CROSS = 3
let tf = tf1-tf2

```

```

meas tran tpr1 WHEN V(in) = mid CROSS = 2
meas tran tpr2 WHEN V(out) = mid CROSS = 2
let tpr = tpr2-tpr1
meas tran tpf1 WHEN V(in) = mid CROSS = 3
meas tran tpf2 WHEN V(out) = mid CROSS = 3
let tpf = tpf2-tpf1
let tp = (tpr + tpf)/2
print tr tf tpr tpf tp
plot V(out) V(in)
wrdata 432.txt V(out)
.endc
.end

```

### 3.2.6.3 $W_p/W_n = 30\mu m/60\mu m$

```

Param Rathour (190070049), CMOS Inverter
.include CMOS.txt           ; Includes NMOS Model
.param Wn = {60u} Wp = {30u} Len = {0.4u}
.param Vd = 3.3
* M drain gate source body cmos
Mn out in gnd gnd cmosn L=Len W=Wn AS={2*Wn*Len} PS={2*Wn+4*Len}
    AD={2*Wn*Len} PD={2*Wn+4*Len}
Mp out in Vdd Vdd cmosp L=Len W=Wp AS={2*Wp*Len} PS={2*Wp+4*Len}
    AD={2*Wp*Len} PD={2*Wp+4*Len}
C1 out gnd 0.05p
Vdd Vdd gnd Vd
Vin in gnd pulse(0 Vd 0 20p 20p 4n 8n)
* .dc Vin 0 Vd 0.01
.tran 1p 30n
.control
let Vddd = 3.3
run
let l = {Vddd*0.1}
let h = {Vddd*0.9}
let mid = {Vddd*0.5}
meas tran tr1 WHEN V(out) = l CROSS = 2
meas tran tr2 WHEN V(out) = h CROSS = 2
let tr = tr2-tr1
meas tran tf1 WHEN V(out) = l CROSS = 3
meas tran tf2 WHEN V(out) = h CROSS = 3
let tf = tf1-tf2
meas tran tpr1 WHEN V(in) = mid CROSS = 2
meas tran tpr2 WHEN V(out) = mid CROSS = 2
let tpr = tpr2-tpr1
meas tran tpf1 WHEN V(in) = mid CROSS = 3
meas tran tpf2 WHEN V(out) = mid CROSS = 3

```

```

let tpf = tpf2-tpf1
let tp = (tpr + tpf)/2
print tr tf tpr tpf tp
plot V(out) V(in)
wrdata 433.txt V(out)
.endc
.end

```

### 3.2.7 CMOS Inverter: Transient Characteristics dependence on $V_{dd}$

#### 3.2.7.1 $V_{dd} = 2V$

```

Param Rathour (190070049), CMOS Inverter
.include CMOS.txt ; Includes NMOS Model
.param Wn = {30u} Wp = {60u} Len = {0.4u}
.param Vd = 2
* M drain gate source body cmos
Mn out in gnd gnd cmosn L=Len W=Wn AS={2*Wn*Len} PS={2*Wn+4*Len}
  AD={2*Wn*Len} PD={2*Wn+4*Len}
Mp out in Vdd Vdd cmosp L=Len W=Wp AS={2*Wp*Len} PS={2*Wp+4*Len}
  AD={2*Wp*Len} PD={2*Wp+4*Len}
C1 out gnd 0.05p
Vdd Vdd gnd Vd
Vin in gnd pulse(0 Vd 0 20p 20p 4n 8n)
* .dc Vin 0 Vd 0.01
.tran 1p 30n
.control
let Vddd = Vd
run
let mid = {Vddd*0.5}
meas tran tpr1 WHEN V(in) = mid CROSS = 2
meas tran tpr2 WHEN V(out) = mid CROSS = 2
let tpr = tpr2-tpr1
meas tran tpf1 WHEN V(in) = mid CROSS = 3
meas tran tpf2 WHEN V(out) = mid CROSS = 3
let tpf = tpf2-tpf1
let tp = (tpr + tpf)/2
print tpr tpf tp
plot V(out) V(in)
wrdata 441.txt V(out)
.endc
.end

```

#### 3.2.7.2 $V_{dd} = 2.3V$

```

Param Rathour (190070049), CMOS Inverter
.include CMOS.txt           ; Includes NMOS Model
.param Wn = {30u} Wp = {60u} Len = {0.4u}
.param Vd = 2.3
* M drain gate source body cmos
Mn out in gnd gnd cmosn L=Len W=Wn AS={2*Wn*Len} PS={2*Wn+4*Len}
    AD={2*Wn*Len} PD={2*Wn+4*Len}
Mp out in Vdd Vdd cmosp L=Len W=Wp AS={2*Wp*Len} PS={2*Wp+4*Len}
    AD={2*Wp*Len} PD={2*Wp+4*Len}
C1 out gnd 0.05p
Vdd Vdd gnd Vd
Vin in gnd pulse(0 Vd 0 20p 20p 4n 8n)
* .dc Vin 0 Vd 0.01
.tran 1p 30n
.control
let Vddd = Vd
run
let mid = {Vddd*0.5}
meas tran tpr1 WHEN V(in) = mid CROSS = 2
meas tran tpr2 WHEN V(out) = mid CROSS = 2
let tpr = tpr2-tpr1
meas tran tpf1 WHEN V(in) = mid CROSS = 3
meas tran tpf2 WHEN V(out) = mid CROSS = 3
let tpf = tpf2-tpf1
let tp = (tpr + tpf)/2
print tpr tpf tp
plot V(out) V(in)
wrdata 442.txt V(out)
.endc
.end

```

### 3.2.7.3 $V_{dd} = 2.6V$

```

Param Rathour (190070049), CMOS Inverter
.include CMOS.txt           ; Includes NMOS Model
.param Wn = {30u} Wp = {60u} Len = {0.4u}
.param Vd = 2.6
* M drain gate source body cmos
Mn out in gnd gnd cmosn L=Len W=Wn AS={2*Wn*Len} PS={2*Wn+4*Len}
    AD={2*Wn*Len} PD={2*Wn+4*Len}
Mp out in Vdd Vdd cmosp L=Len W=Wp AS={2*Wp*Len} PS={2*Wp+4*Len}
    AD={2*Wp*Len} PD={2*Wp+4*Len}
C1 out gnd 0.05p
Vdd Vdd gnd Vd
Vin in gnd pulse(0 Vd 0 20p 20p 4n 8n)

```

```

* .dc Vin 0 Vd 0.01
.tran 1p 30n
.control
let Vddd = Vd
run
let mid = {Vddd*0.5}
meas tran tpr1 WHEN V(in) = mid CROSS = 2
meas tran tpr2 WHEN V(out) = mid CROSS = 2
let tpr = tpr2-tpr1
meas tran tpf1 WHEN V(in) = mid CROSS = 3
meas tran tpf2 WHEN V(out) = mid CROSS = 3
let tpf = tpf2-tpf1
let tp = (tpr + tpf)/2
print tpr tpf tp
plot V(out) V(in)
wrdata 443.txt V(out)
.endc
.end

```

#### 3.2.7.4 $V_{dd} = 3V$

```

Param Rathour (190070049), CMOS Inverter
.include CMOS.txt ; Includes NMOS Model
.param Wn = {30u} Wp = {60u} Len = {0.4u}
.param Vd = 3
* M drain gate source body cmos
Mn out in gnd gnd cmosn L=Len W=Wn AS={2*Wn*Len} PS={2*Wn+4*Len}
    AD={2*Wn*Len} PD={2*Wn+4*Len}
Mp out in Vdd Vdd cmosp L=Len W=Wp AS={2*Wp*Len} PS={2*Wp+4*Len}
    AD={2*Wp*Len} PD={2*Wp+4*Len}
C1 out gnd 0.05p
Vdd Vdd gnd Vd
Vin in gnd pulse(0 Vd 0 20p 20p 4n 8n)
* .dc Vin 0 Vd 0.01
.tran 1p 30n
.control
let Vddd = Vd
run
let mid = {Vddd*0.5}
meas tran tpr1 WHEN V(in) = mid CROSS = 2
meas tran tpr2 WHEN V(out) = mid CROSS = 2
let tpr = tpr2-tpr1
meas tran tpf1 WHEN V(in) = mid CROSS = 3
meas tran tpf2 WHEN V(out) = mid CROSS = 3
let tpf = tpf2-tpf1
let tp = (tpr + tpf)/2

```



```

print tpr tpf tp
plot V(out) V(in)
wrdata 444.txt V(out)
.endc
.end

```

### 3.2.7.5 $V_{dd} = 3.3V$

```

Param Rathour (190070049), CMOS Inverter
.include CMOS.txt ; Includes NMOS Model
.param Wn = {30u} Wp = {60u} Len = {0.4u}
.param Vd = 3.3
* M drain gate source body cmos
Mn out in gnd gnd cmosn L=Len W=Wn AS={2*Wn*Len} PS={2*Wn+4*Len}
    AD={2*Wn*Len} PD={2*Wn+4*Len}
Mp out in Vdd Vdd cmosp L=Len W=Wp AS={2*Wp*Len} PS={2*Wp+4*Len}
    AD={2*Wp*Len} PD={2*Wp+4*Len}
C1 out gnd 0.05p
Vdd Vdd gnd Vd
Vin in gnd pulse(0 Vd 0 20p 20p 4n 8n)
* .dc Vin 0 Vd 0.01
.tran 1p 30n
.control
let Vddd = Vd
run
let mid = {Vddd*0.5}
meas tran tpr1 WHEN V(in) = mid CROSS = 2
meas tran tpr2 WHEN V(out) = mid CROSS = 2
let tpr = tpr2-tpr1
meas tran tpf1 WHEN V(in) = mid CROSS = 3
meas tran tpf2 WHEN V(out) = mid CROSS = 3
let tpf = tpf2-tpf1
let tp = (tpr + tpf)/2
print tpr tpf tp
plot V(out) V(in)
wrdata 445.txt V(out)
.endc
.end

```

## 3.3 Python Code for Plots and Calculations

```

import numpy as np
import matplotlib.pyplot as plt
from scipy import stats
import math

```

```
import pandas as pd
import bisect
```

### 3.3.1 $I_D/V_{DS}$ characteristics of NMOS for different $V_{GS}$

```
V_GS = np.arange(2.5, 4.5, 0.5)

V_DS = []
I_D = []

fig1, ax1 = plt.subplots()
ax1.set_xlabel('Voltage  $V_{DS}$  (in V)')
ax1.set_ylabel('Current  $I_{D}$  (in mA)')
ax1.set_title('$I_D-V_{DS}$ Characteristics of NMOS at different  $V_{GS}$ ')

for i in range(len(V_GS)):
    data = pd.read_csv('E:\Program_Files\Spice64\EE236\Lab6\\11' + str(i+1)
                      + '.txt', header = None, skipinitialspace=True,
                      delim_whitespace=True)
    V_DS.append(data[0])
    I_D.append(data[1])
    ax1.plot(V_DS[i], 1000*I_D[i], '-o', markersize=0.01)
ax1.legend(V_GS)
fig1.set_dpi(150)
fig1.savefig('111.pdf')

slopes = []
for i in range(len(V_GS)):
    slope = []
    for j in range(len(V_DS[i])-1):
        slope.append((I_D[i][j+1]-I_D[i][j])/(V_DS[i][j+1]-V_DS[i][j]))
    slopes.append(slope)
# slopes[0]

slope_min = np.zeros(len(V_GS))
slope_max = np.zeros(len(V_GS))
for i in range(len(V_GS)):
    slope_min[i] = min(slopes[i])
    slope_max[i] = max(slopes[i])
print(slope_min)
print(slope_max)

r_DS = [1/i for i in slope_max]
print("r_DS", r_DS)
r_0 = [1/i for i in slope_min]
print("r_0", r_0)
```

```

fig1, ax1 = plt.subplots()
ax1.set_xlabel('Index of exported data')
ax1.set_ylabel('Slope')
ax1.set_title('Slope Distribution')
for i in range(len(V_DS[0])-1):
    plt.scatter(i, (V_DS[0][i+1]-V_DS[0][i])/(I_D[0][i+1]-I_D[0][i]))
fig1.set_dpi(150)
fig1.savefig('121.pdf')

y_intercepts = np.zeros(len(V_GS))
slope_fit = np.zeros(len(V_GS))
for i in range(len(V_GS)):
    slope, intercept, r_value, p_value, std_err =
        stats.linregress(V_DS[i][-2:], I_D[i][-2:])
    y_intercepts[i] = intercept
    slope_fit[i] = slope
print(slope_fit)
print(y_intercepts)

V_A = np.zeros(len(V_GS))
R_0 = np.zeros(len(V_GS))
fig1, ax1 = plt.subplots()
ax1.set_xlabel('Voltage (in V)')
ax1.set_ylabel('Current (in mA)')
ax1.set_ylim([0,3])
ax1.set_title('$I_D$-$V_{DS}$ Characteristics of NMOS at different $V_{GS}$')
fig1.set_dpi(150)
intersect = -35
x = np.arange(intersect,5,0.01)
for i in range(len(V_GS)):
    ax1.plot(V_DS[i], 1000*I_D[i], '-o', markersize=0.01)
for i in range(len(V_GS)):
    ax1.plot(x, 1000*(slope_fit[i]*x+y_intercepts[i]), '--o', markersize=0.01)
    V_A[i] = -y_intercepts[i]/slope_fit[i]
    R_0[i] = 1/slope_fit[i]
print(V_A)
print(np.mean(V_A))
print(R_0)
ax1.legend(V_GS)
fig1.savefig('122.pdf')

```

### 3.3.2 $I_D/V_{GS}$ characteristics of NMOS for different $V_{DS}$

```

data = pd.read_csv('E:\Program_Files\Spice64\EE236\Lab6\211.txt',
                  header = None, skipinitialspace=True, delim_whitespace=True)

```

```

V_GS = data[0]
I_D = data[1]

fig1, ax1 = plt.subplots()
ax1.set_xlabel('Voltage $V_{GS}$ (in V)')
ax1.set_ylabel('Current $I_D$ (in mA)')
ax1.set_title('$I_D$-$V_{GS}$ Characteristics of NMOS at $V_{DS}$=200mV$')
# ax1.legend(V_GS)
fig1.set_dpi(150)
slope, y_intercept, r_value, p_value, std_err =
    stats.linregress(V_GS[-2:], 1000*I_D[-2:])
ax1.plot(V_GS, slope*V_GS + y_intercept, '-o', markersize=0.01)
ax1.plot(V_GS, 1000*I_D, '-o', markersize=0.01)
print(y_intercept)
V_T = -y_intercept/slope
print("V_T =", V_T)
g_m = slope
print("g_m =", g_m) # in m mhos
fig1.savefig('21.pdf')

data = pd.read_csv('E:\Program_Files\Spice64\EE236\Lab6\221.txt',
                  header = None, skipinitialspace=True, delim_whitespace=True)
V_GS = data[0]
I_D = data[1]
I_D_sqrt = [math.sqrt(i) for i in I_D]
fig1, ax1 = plt.subplots()
ax1.set_xlabel('Voltage $V_{GS}$ (in V)')
ax1.set_ylabel('Current $I_D$ (in mA)')
ax1.set_title('$I_D$-$V_{GS}$ Characteristics of NMOS at $V_{DS}$=5V$')
# ax1.legend(V_GS)
fig1.set_dpi(150)
ax1.plot(V_GS, 1000*I_D, '-o', markersize=0.01)

fig2, ax2 = plt.subplots()
ax2.set_xlabel('Voltage $V_{GS}$ (in V)')
ax2.set_ylabel('$\sqrt{Current}$ $\sqrt{I_D}$ (in mA)')
ax2.set_title('$\sqrt{I_D}$-$V_{GS}$ Characteristics of NMOS at $V_{DS}$=5V$')
slope, y_intercept, r_value, p_value, std_err =
    stats.linregress(V_GS[-2:], (I_D_sqrt[-2:]))
ax2.plot(V_GS, slope*V_GS + y_intercept, '-o', markersize=0.01)
ax2.plot(V_GS, I_D_sqrt, '-o', markersize=0.01)
fig2.set_dpi(150)
V_T = -y_intercept/slope
print("V_T =", V_T)
K = 1000*2*slope**2
print("K =", K) # mA/V^2
# print(V_GS[300])

```

```

g_m = 1000*(I_D[301]-I_D[300]) / (V_GS[301]-V_GS[300])
print("g_m =", g_m) # in m mhos
fig1.savefig('221.pdf')
fig2.savefig('222.pdf')
# fig2.legend(["Characteristics", "Extrapolation"])

```

### 3.3.3 $I_D/V_{GS}$ characteristics of NMOS for different $V_{SB}$

```

V_SB = np.arange(0,5,1)

V_GS = []
I_D = []

fig1, ax1 = plt.subplots()
ax1.set_xlabel('Voltage $V_{GS}$ (in V)')
ax1.set_ylabel('Current $I_D$ (in mA)')
ax1.set_title('$I_D$-$V_{GS}$ Characteristics of NMOS at $V_{DS}$=200mV$')

for i in range(len(V_SB)):
    data = pd.read_csv('E:\Program_Files\Spice64\EE236\Lab6\\31' + str(i+1)
                      + '.txt', header = None, skipinitialspace=True,
                      delim_whitespace=True)
    V_GS.append(data[0])
    I_D.append(data[1])
    ax1.plot(V_GS[i], 1000*I_D[i], '-o', markersize=0.01)
ax1.legend(V_SB)
fig1.set_dpi(150)
fig1.savefig('311.pdf')

y_intercepts = np.zeros(len(V_SB))
slope_fit = np.zeros(len(V_SB))
for i in range(len(V_SB)):
    slope, intercept, r_value, p_value, std_err =
        stats.linregress(V_GS[i][-2:], I_D[i][-2:])
    y_intercepts[i] = intercept
    slope_fit[i] = slope
print(slope_fit)
print(y_intercepts)

V_T = np.zeros(len(V_SB))
fig1, ax1 = plt.subplots()
ax1.set_xlabel('Voltage $V_{GS}$ (in V)')
ax1.set_xlim([0,5])
ax1.set_ylabel('Current $I_D$ (in mA)')
ax1.set_ylim([-0.2,0.4])
ax1.set_title('$I_D$-$V_{GS}$ Characteristics of NMOS at $V_{DS}$=200mV$')

```

```

fig1.set_dpi(150)
intersect = -10
for i in range(len(V_SB)):
    x = np.arange(intersect, -y_intercepts[i]/slope_fit[i], 0.01)
    ax1.plot(V_GS[i], 1000*I_D[i], '-o', markersize=0.01)
    V_T[i] = -y_intercepts[i]/slope_fit[i]
for i in range(len(V_SB)):
    ax1.plot(x, 1000*(slope_fit[i]*x+y_intercepts[i]), '--o', markersize=0.01)
print(V_T)
ax1.legend(V_SB)
fig1.savefig('312.pdf')

gamma = []
phi_s = 0.9
V_T0 = V_T[0]
for i in range(1, len(V_SB)):
    gamma.append((V_T[i] - V_T0)/(math.sqrt(phi_s+V_SB[i]) - math.sqrt(phi_s)))
gamma

gamma_avg = np.mean(gamma)
gamma_avg

V_Ta = np.zeros(len(V_SB))
for i in range(len(V_SB)):
    V_Ta[i] = V_T0 + gamma_avg*(math.sqrt(phi_s+V_SB[i]) - math.sqrt(phi_s))

fig1, ax1 = plt.subplots()
ax1.set_xlabel('Voltage $V_{T}$ (in V)')
ax1.set_ylabel('Voltage $V_{SB}$ (in V)')
ax1.plot(V_SB, V_T, '--om')
ax1.plot(V_SB, V_Ta, '--c')
fig1.set_dpi(150)
plt.legend(["Actual $V_T$", "Extrapolated $V_T$ using $\gamma_{avg}$"])
fig1.savefig('32.pdf')

```

### 3.4 CMOS Inverter Voltage Transfer Characteristics

```

data = pd.read_csv('E:\Program_Files\Spice64\EE236\Lab6\411.txt',
                  header = None, skipinitialspace=True, delim_whitespace=True)
V_out = data[1]
V_in = data[0]

fig1, ax1 = plt.subplots()
ax1.set_xlabel('Voltage $V_{in}$ (in V)')
ax1.set_ylabel('Voltage $V_{out}$ (in V)')
ax1.set_title('Voltage Transfer Characteristics, CMOS Inverter')

```

```

# ax1.legend(V_GS)
fig1.set_dpi(150)
ax1.plot(V_in, V_out, '-o', markersize=0.01)
fig1.savefig('411.pdf')

fig1, ax1 = plt.subplots()
ax1.set_xlabel('Index of exported data')
ax1.set_ylabel('Slope')
ax1.set_title('Slope Distribution')

maxi = 0
maxe = 0

for i in range(len(V_in)-1):
    if V_out[i+1] != V_out[i]:
        slope = abs((V_out[i+1]-V_out[i])/(V_in[i+1]-V_in[i]))
        if (maxe < slope):
            maxe = slope
            maxi = i
        plt.scatter(i,slope)
fig1.set_dpi(150)
fig1.savefig('412.pdf')
print(maxi)
print(V_in[maxi])

V_out = []
V_in = []

fig1, ax1 = plt.subplots()
ax1.set_xlabel('Voltage $V_{in}$ (in V)')
ax1.set_ylabel('Voltage $V_{out}$ (in V)')
ax1.set_title('Voltage Transfer Characteristics, CMOS Inverter')

for i in range(3):
    data = pd.read_csv('E:\Program_Files\Spice64\EE236\Lab6\\41' + str(i+1)
                      + '.txt', header = None, skipinitialspace=True,
                      delim_whitespace=True)
    V_out.append(data[1])
    V_in.append(data[0])
    ax1.plot(V_in[i], V_out[i], '-o', markersize=0.01)
ax1.legend(["$W_p/W_n = 60\mu m/30\mu m$", "$W_p/W_n = 60\mu m/60\mu m$",
           "$W_p/W_n = 30\mu m /60\mu m$"])
fig1.set_dpi(150)
fig1.savefig('421.pdf')

for i in range(3):
    maxi = 0

```

```

maxe = 1e5
for j in range(len(V_in[i])):
    diff = abs(V_out[i][j] - V_in[i][j])
    if maxe > diff:
        maxe = diff
        maxi = j
print(V_in[i][maxi], (V_out[i][maxi]))
print("Switching Threshold =", (V_in[i][maxi] + (V_out[i][maxi]))/2)

for i in range(3):
    maxi = 0
    maxe = 0
    for j in range(len(V_in[i])-1):
        if V_out[i][j+1] != V_out[i][j]:
            slope = abs((V_out[i][j+1]-V_out[i][j])/(V_in[i][j+1]-V_in[i][j]))
            if (maxe < slope):
                maxe = slope
                maxi = j
    print(V_in[i][maxi], (V_out[i][maxi]))
    print("Switching Threshold =", (V_in[i][maxi] + (V_out[i][maxi]))/2)

V_out = []
V_in = []
V_dd = [1.5, 3, 3.3]

fig1, ax1 = plt.subplots()
ax1.set_xlabel('Voltage $V_{in}$ (in V)')
ax1.set_ylabel('Voltage $V_{out}$ (in V)')
ax1.set_title('Voltage Transfer Characteristics, CMOS Inverter')

for i in range(3):
    data = pd.read_csv('E:\Program_Files\Spice64\EE236\Lab6\\42' +
                      str(i+1) + '.txt', header = None, skipinitialspace=True,
                      delim_whitespace=True)
    V_out.append(data[1])
    V_in.append(data[0])
    ax1.plot(V_in[i], V_out[i], '-o', markersize=0.01)
ax1.legend(V_dd)
fig1.set_dpi(150)
fig1.savefig('422.pdf')

V_out = []
V_in = []
V_dd = [1.5, 2, 2.5, 3, 3.3]

fig1, ax1 = plt.subplots()
ax1.set_xlabel('Voltage $V_{in}$ (in V)')

```



```

ax1.set_ylabel('Voltage $V_{out}$ (in V)')
ax1.set_title('Voltage Transfer Characteristics, CMOS Inverter')

for i in range(5):
    data = pd.read_csv('E:\Program_Files\Spice64\EE236\Lab6\\42' + str(i+1)
                      + '.txt', header = None, skipinitialspace=True,
                      delim_whitespace=True)
    V_out.append(data[1])
    V_in.append(data[0])
    ax1.plot(V_in[i], V_out[i], '-o', markersize=0.01)
ax1.legend(V_dd)
fig1.set_dpi(150)
fig1.savefig('422.pdf')

```

### 3.4.1 CMOS Inverter Transient Characteristics

```

V_d = [2, 2.3, 2.6, 3, 3.3]
t_p_f = [2.969600e-11, 3.222300e-11, 3.363000e-11, 3.471800e-11, 3.523700e-11]
t_p_r = [9.539800e-11, 6.777200e-11, 5.253800e-11, 4.023600e-11, 3.407600e-11]
t_p = [6.254700e-11, 4.999750e-11, 4.308400e-11, 3.747700e-11, 3.465650e-11]
fig1, ax1 = plt.subplots()
ax1.plot(V_d, t_p_f)
ax1.plot(V_d, t_p_r)
ax1.plot(V_d, t_p)
ax1.set_xlabel("$V_d$ (in V)")
ax1.set_ylabel("$t$ (in s)")
ax1.legend(["$t_{p_f}$", "$t_{p_r}$", "$t_p$"])
fig1.set_dpi(150)
fig1.savefig('43.pdf')

```

## 4 Experiment completion status

Completed everything in Lab successfully.

## 5 Questions for reflection

Please see my Design and Simulation Result sections for these comments.  
Overall, the lab was good. Thanks!