

# EE236: Experiment 3

## $I/V$ and $C/V$ Characteristics of Solar Cell

Param Rathour, 190070049  
Spring Semester, 2021-22

### Contents

<b>1</b>	<b>Overview of the experiment</b>	<b>1</b>
1.1	Aim of the experiment . . . . .	2
1.2	Methods . . . . .	2
<b>2</b>	<b>Design</b>	<b>2</b>
<b>3</b>	<b>Simulation results</b>	<b>4</b>
3.1	Plots . . . . .	4
3.1.1	$I/V$ Characteristics of Solar . . . . .	4
3.1.2	Measurement of $V_{OC}$ and $I_{SC}$ and fill factor of solar cell . . . . .	6
3.1.3	Solar Cell $C/V$ Measurement . . . . .	7
3.2	Code Snippets . . . . .	7
3.2.1	$I/V$ Characteristics of Solar . . . . .	7
3.2.1.1	$I_L = 0$ . . . . .	7
3.2.1.2	$I_L = 8mA$ . . . . .	8
3.2.1.3	$I_L = 10mA$ . . . . .	8
3.2.2	Measurement of $V_{OC}$ and $I_{SC}$ and factor of solar cell . . . . .	9
3.2.2.1	$I_L = 8mA$ . . . . .	9
3.2.2.2	$I_L = 10mA$ . . . . .	10
3.2.2.3	$C/V$ characteristics of a Solar Cell . . . . .	10
3.2.3	Code for Plots . . . . .	11
<b>4</b>	<b>Experiment completion status</b>	<b>12</b>
<b>5</b>	<b>Questions for reflection</b>	<b>12</b>

## 1 Overview of the experiment

This report contains my approach to the experiment, the circuit's design with the relevant simulation code and output plots.

## 1.1 Aim of the experiment

- To plot and understand  $I/V$  characteristics of solar cell under different lighting conditions and calculate fill factor
- To plot and understand  $C/V$  characteristics of solar cell and calculate built-in potential and doping concentration


## 1.2 Methods

First a comparison between different lighting conditions was made using the parameters (ideality factor) from the  $I/V$  characteristics of solar cell.


Then,  $C/V$  characteristics of a Solar Cell was calculated using the given circuit made of inverting summing amplifier and current to voltage converter and the parameters were calculated appropriately.
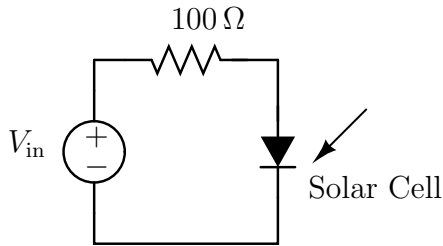
## 2 Design

$I/V$  characteristics circuit was taken from experiment 3 handout (Figure 1a). Voltage was varied from  $-2$  to  $+2$ .



(a) For  $I/V$  characteristics

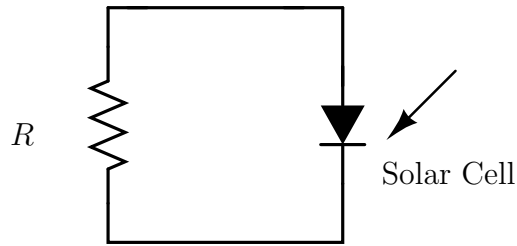

(b) Measurement of  $V_{OC}$  and  $I_{SC}$

Analytically,

$$I = I_0 \left( e^{\frac{q \cdot V_D}{\eta k T}} - 1 \right) - I_L \quad (1)$$

By taking natural logarithm of  $I$  and neglecting  $-1$ , we get  $\log(I + I_L)/V$  characteristics

$$\ln(I + I_L) = \ln(I_0) + \frac{q \cdot V}{\eta k T} \rightarrow \ln(I + I_L) = \underbrace{\frac{q}{\eta k T}}_{\text{slope}} \cdot V + \underbrace{\ln(I_0)}_{\text{y-intercept}} \quad (2)$$

This graph is a straight line in some range of  $I, V$ . We can calculate its slope to get  $\eta$  and y-intercept by interpolating that straight line to get  $I_S$

$$\text{slope} = \frac{\ln(I + I_L)_2 - \ln(I + I_L)_1}{V_2 - V_1} = \frac{1}{\eta V_T} \rightarrow \eta = \frac{1}{V_T} \left( \frac{V_{D_2} - V_{D_1}}{\ln(I + I_L)_2 - \ln(I + I_L)_1} \right) \quad (3)$$

Then, the circuit for measurement of  $V_{OC}$  and  $I_{SC}$  was also taken from slides (Figure 1b)

Here, all parameters were calculated from NGSPICE commands itself.

$I_{SC}$  is maximum current through the cell.

$V_{OC}$  is maximum voltage across the cell.

$I_{MP}$ ,  $V_{MP}$  and  $P_{MP}$  were taken from  $P_R - V_D$  graph.

$$\text{Fill Factor} = \frac{I_{MP} \cdot V_{MP}}{I_{SC} \cdot V_{OC}}$$

The circuit for  $C/V$  measurement is taken from slides too (Figure 2),

Voltage dc1 is varied from 0 to 2V and  $V_{sin}$  is 1V peak to peak 1kHz.

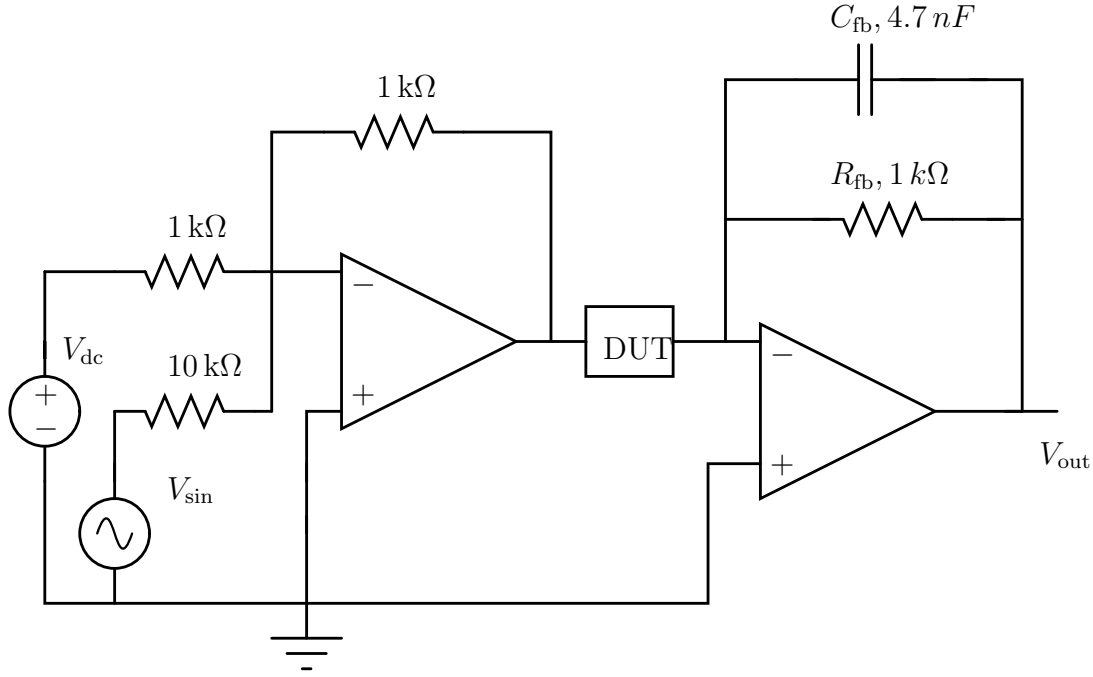


Figure 2:  $C/V$  Measurement

In  $C_{DUT}$  vs  $V_{dc}$ ,  $C$  is calculated using  $V_{out}$  by below equation

$$\left| \frac{V_{out}}{V_{DUT}} \right| = \frac{C_{DUT}}{C_{fb}} \cdot \frac{1}{\sqrt{1 + \frac{1}{(\omega R_{fb} \cdot C_{fb})^2}}}$$

So,

$$C_{DUT} = \left| \frac{V_{out}}{V_{DUT}} \right| \cdot C_{fb} \cdot \sqrt{1 + \frac{1}{(\omega R_{fb} \cdot C_{fb})^2}} \quad (4)$$

$C$  is normalised capacitance =  $\frac{C_{DUT}}{\text{Area}}$ , where area =  $4cm \cdot 4cm$

Built-in potential and doping concentration were calculated using  $1/C^2$  vs  $V_{DUT}$  plot and the following equation

$$\frac{1}{C^2} = \underbrace{\frac{2}{q\epsilon N_D} \cdot V_{bi}}_{\text{y-intercept}} - \underbrace{\frac{2}{q\epsilon N_D} \cdot V_R}_{\text{slope}} \quad (5)$$

## 3 Simulation results

### 3.1 Plots


#### 3.1.1 $I/V$ Characteristics of Solar

Ideality factor for the three cases are


$$I_L = 0 \text{ , } \eta = 3.44781$$

$$I_L = 8mA \text{ , } \eta = 4.026876$$

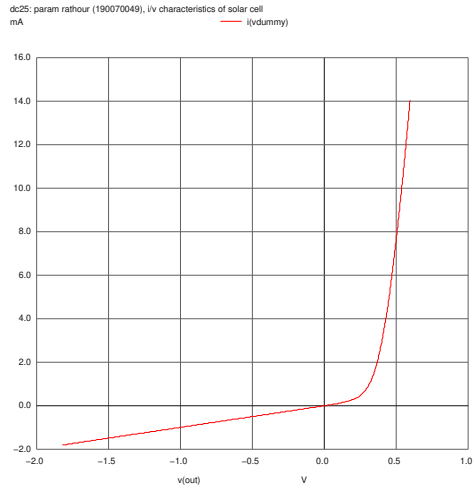
$$I_L = 10mA \text{ , } \eta = 4.151296$$




(a)  $I/V$  when  $I_L = 0$

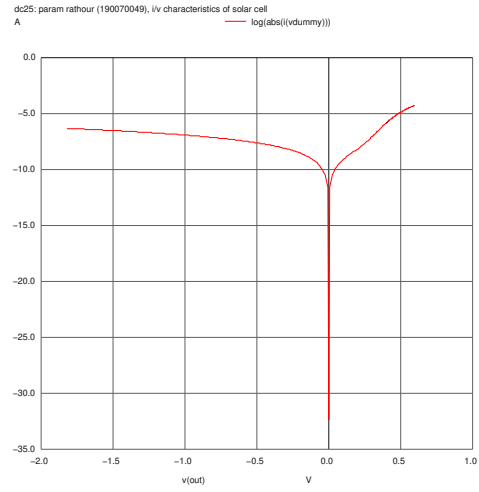


(b)  $\log I/V$  when  $I_L = 0$

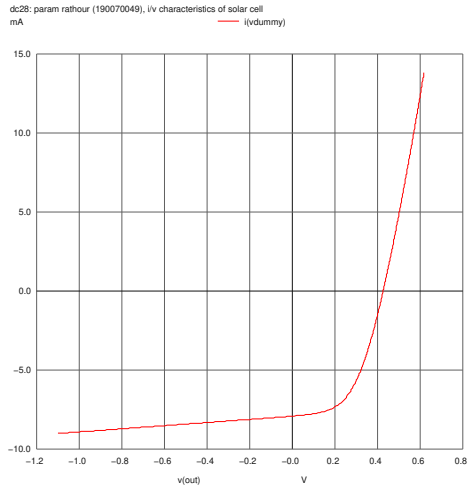


(c)  $I/V$  when  $I_L = 8mA$

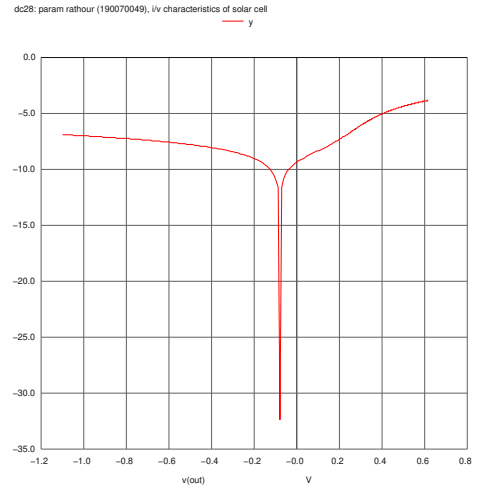

(d)  $\log I/V$  when  $I_L = 8mA$

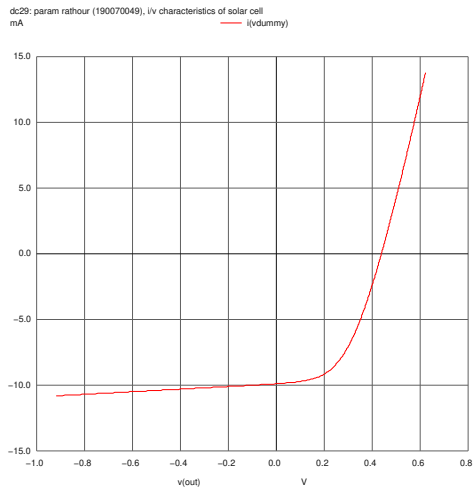

(e)  $I/V$  when  $I_L = 10mA$

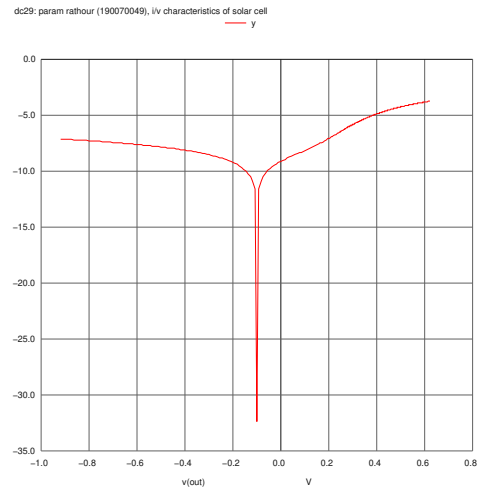


(f)  $\log I/V$  when  $I_L = 10mA$

Figure 3: I/V Characteristics of Solar Cell


### 3.1.2 Measurement of $V_{OC}$ and $I_{SC}$ and fill factor of solar cell

$I_L$ (in mA)	$I_{SC}$ (in mA)	$V_{OC}$ (in mV)	$V_{MP}$ (in mV)	$I_{MP}$ (in mA)	Fill Factor
8	7.90431	412.0659	276.429	6.19565	0.5312704
10	9.87702	424.9854	275	7.78378	0.5116530


Table 1: Band Gap for different diodes using Peak Emission Wavelength

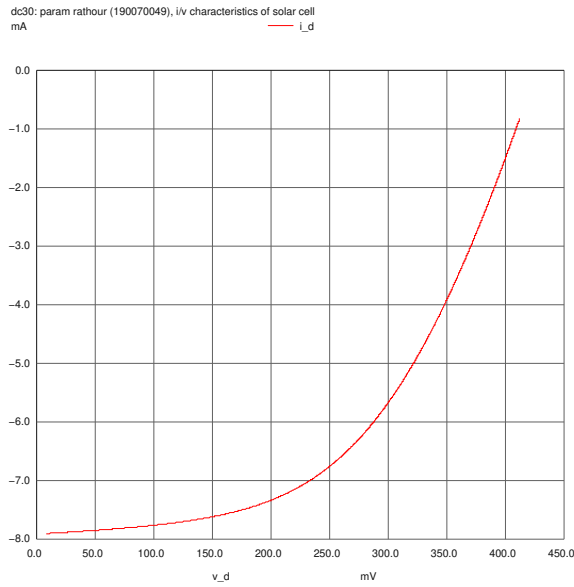


(a)  $I_D - V_D$  when  $I_L = 8$  mA

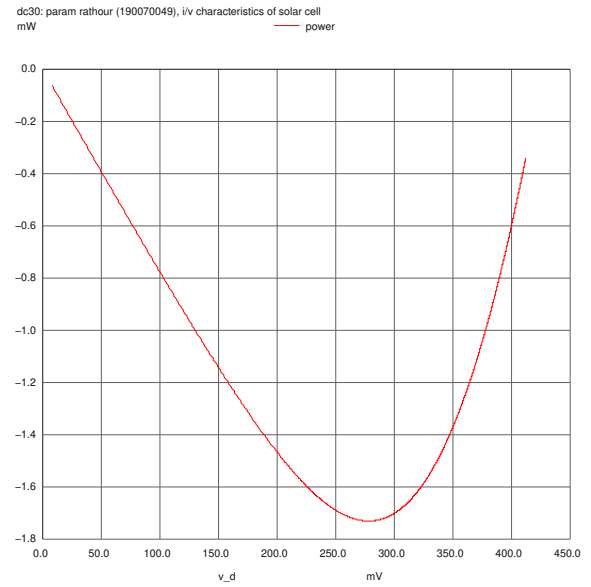

(b)  $P_R - V_D$  when  $I_L = 8$  mA

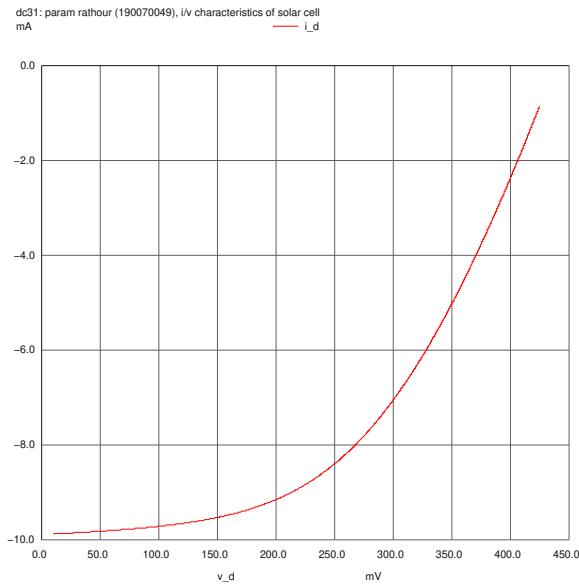

(c)  $I_D - V_D$  when  $I_L = 10$  mA

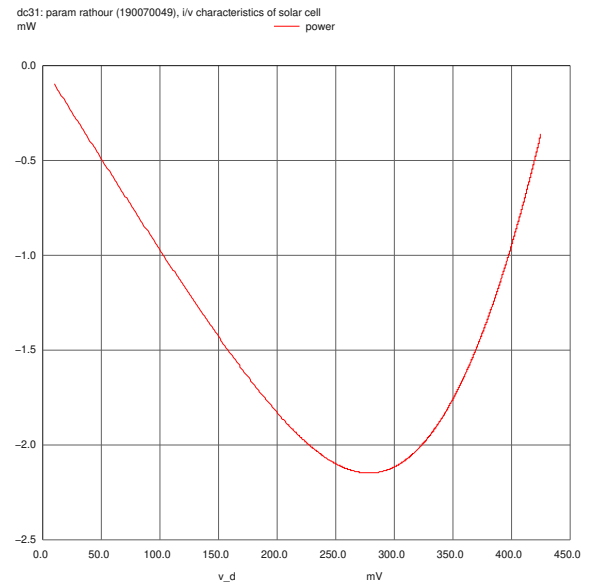


(d)  $P_R - V_D$  when  $I_L = 10$  mA

Figure 4: Measurement of  $V_{OC}$  and  $I_{SC}$  and factor of solar cell
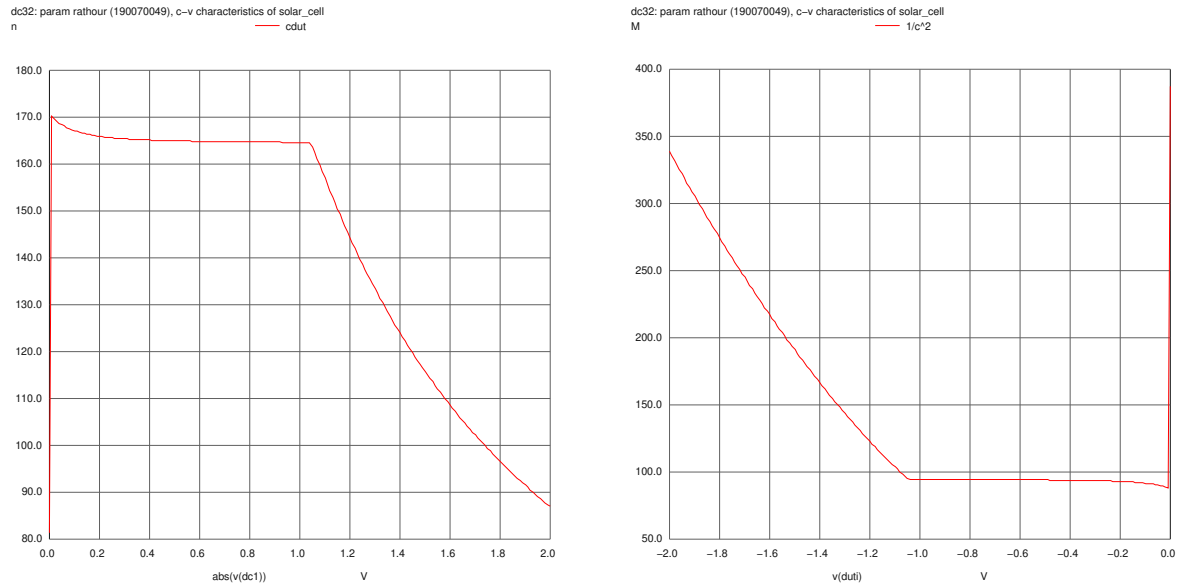
### 3.1.3 Solar Cell $C/V$ Measurement

$$N_D = 4.475974 \cdot 10^{14} \text{ atoms} \cdot \text{cm}^{-3} \quad V_{bi} = 0.782769V$$



(a)  $C_{DUT}$  vs  $V_{dc}$

(b)  $1/C^2$  vs  $V_{DUT}$

Figure 5: Solar Cell  $C/V$  Measurement

## 3.2 Code Snippets

### 3.2.1 $I/V$ Characteristics of Solar

#### 3.2.1.1 $I_L = 0$

Param Rathour (190070049),  $I/V$  characteristics of Solar Cell

```
.include Solar_Cell.txt ; Includes Solar Cell Model

R1 mid out 100
X1 out gnd solar_cell IL_val = 0 ; Solar Cell
Vin in gnd dc 0 ; DC source Vin
Vdummy in mid 0 ;
.dc Vin -2 2 0.01 ; DC Analysis
.control
run
plot I(Vdummy) vs V(out)
plot log(abs(I(Vdummy))) vs V(out)
let VD1 = 0.15
let VD2 = 0.4
meas dc ID1 FIND I(Vdummy) WHEN V(out) = VD1
meas dc ID2 FIND I(Vdummy) WHEN V(out) = VD2
```

```

let lnID1 = log(ID1)
let lnID2 = log(ID2)
let slope = (lnID2 - lnID1) / (VD2 - VD1)
* let yintercept = lnID1 - slope * VD1
let eta = (VD2 - VD1) / ((26/1000) * (lnID2 - lnID1))
print eta                                ; , exp(yintercept)

hardcopy 1a1.eps I(Vdummy) vs V(out)
hardcopy 1a2.eps log(abs(I(Vdummy))) vs V(out)
.endc
.end

```

### 3.2.1.2 $I_L = 8mA$

```

Param Rathour (190070049), I/V characteristics of Solar Cell

.include Solar_Cell.txt                ; Includes Solar Cell Model

R1 mid out 100
X1 out gnd solar_cell IL_val = 8e-3    ; Solar Cell
Vin in gnd dc 0                        ; DC source Vin
Vdummy in mid 0                        ;
.dc Vin -2 2 0.01                      ; DC Analysis
.control
run
plot I(Vdummy) vs V(out)
let y = log({abs(I(Vdummy))+8m})
plot y vs V(out)
let VD1 = 0
let VD2 = 0.55
meas dc lnID1 FIND y WHEN V(out) = VD1
meas dc lnID2 FIND y WHEN V(out) = VD2
let slope = (lnID2 - lnID1) / (VD2 - VD1)
* let yintercept = lnID1 - slope * VD1
let eta = 1 / ((26/1000)*slope)
print eta                                ; , exp(yintercept)

hardcopy 1b1a.eps I(Vdummy) vs V(out)
hardcopy 1b1b.eps y vs V(out)
.endc
.end

```

### 3.2.1.3 $I_L = 10mA$



Param Rathour (190070049), I/V characteristics of Solar Cell

```
.include Solar_Cell.txt                ; Includes Solar Cell Model

R1 mid out 100
X1 out gnd solar_cell IL_val = 10e-3   ; Solar Cell
Vin in gnd dc 0                        ; DC source Vin
Vdummy in mid 0                        ;
.dc Vin -2 2 0.01                      ; DC Analysis
.control
run
plot I(Vdummy) vs V(out)
let y = log({abs(I(Vdummy))+10m}))
plot y vs V(out)
let VD1 = 0
let VD2 = 0.55
meas dc lnID1 FIND y WHEN V(out) = VD1
meas dc lnID2 FIND y WHEN V(out) = VD2
let slope = (lnID2 - lnID1) / (VD2 - VD1)
* let yintercept = lnID1 - slope * VD1
let eta = 1 / ((26/1000)*slope)
print eta                               ; , exp(yintercept)

hardcopy 1b2a.eps I(Vdummy) vs V(out)
hardcopy 1b2b.eps y vs V(out)
.endc
.end
```

### 3.2.2 Measurement of $V_{OC}$ and $I_{SC}$ and factor of solar cell

#### 3.2.2.1 $I_L = 8mA$

Param Rathour (190070049), I/V characteristics of Solar Cell

```
.include Solar_Cell.txt                ; Includes Solar Cell Model

R1 in out 0
X1 out gnd solar_cell IL_val = 8e-3    ; Solar Cell
Vdummy in gnd 0                        ;
.dc R1 1 500 0.1                      ; DC Analysis
.control
run
let I_D = -I(Vdummy)
let V_D = V(out)
let Power = I_D*V_D
plot I_D vs V_D
```

```

plot Power vs V_D
let I_SC = minimum(I_D)
let V_OC = maximum(V_D)
let Pmax = minimum(Power)
let FF = Pmax / (I_SC*V_OC)
print I_SC V_OC FF
hardcopy 23a1.eps I_D vs V_D
hardcopy 23a2.eps Power vs V_D
.endc
.end

```

### 3.2.2.2 $I_L = 10mA$

```

Param Rathour (190070049), I/V characteristics of Solar Cell

.include Solar_Cell.txt                ; Includes Solar Cell Model

R1 in out 0
X1 out gnd solar_cell IL_val = 10e-3   ; Solar Cell
Vdummy in gnd 0                       ;
.dc R1 1 500 0.1                      ; DC Analysis
.control
run
let I_D = -I(Vdummy)
let V_D = V(out)
let Power = I_D*V_D
plot I_D vs V_D
plot Power vs V_D
let I_SC = minimum(I_D)
let V_OC = maximum(V_D)
let Pmax = minimum(Power)
let FF = Pmax / (I_SC*V_OC)
print I_SC V_OC FF
hardcopy 23b1.eps I_D vs V_D
hardcopy 23b2.eps Power vs V_D
.endc
.end

```

### 3.2.2.3 $C/V$ characteristics of a Solar Cell

```

Param Rathour (190070049), C-V characteristics of solar_cell

.include Solar_Cell.txt                ; Includes Solar Cell Model
.include TL071.cir                    ; Includes OpAmp Model

```

```

Vdc dc1 gnd dc 0
Vin in gnd sin(0 0.5 1k 0 0) ; Source Vin
Vp1 p1 gnd dc 12
Vn1 n1 gnd dc -12
Vp2 p2 gnd dc 12
Vn2 n2 gnd dc -12
R1 in ni1 10k
R2 dc1 ni1 1k
X1 gnd ni1 p1 n1 duti TL071
RF ni1 duti 1k
X2 duti duto solar_cell IL_val = 0 ; Solar Cell
RFB duto out 10k
CFB duto out 4.7n
X3 gnd duto p2 n2 out TL071
.dc Vdc 0 2 0.01 ; DC Analysis
.control
run
let pi = 3.1415
let k1 = 4.7n*(sqrt(1+1/(2*pi*1k*10k*4.7n)^2))
let Cdut = abs({k1* V(out)/V(duti)})
plot Cdut vs abs(V(dc1))
let k2 = 2/(((8.85e-12)*11.68)*(1.602e-19))
let area = (4e-2)^2
let C = Cdut / area
let y = 1/C^2
plot 1/C^2 vs V(duti)
let VD1 = -1.4
let VD2 = -1.8
meas dc C1 FIND y WHEN V(duti) = VD1
meas dc C2 FIND y WHEN V(duti) = VD2
let slope = (C2 - C1) / (VD2 - VD1)
print slope
let ND = k2/abs(slope)
print ND
let yintercept = C1 - slope*VD1
let Vbi = yintercept*ND/k2
print Vbi
hardcopy 4a.eps Cdut vs abs(V(dc1))
hardcopy 4b.eps 1/C^2 vs V(duti)
.endc
.end

```

### 3.2.3 Code for Plots

```

set hcopydevtype=postscript
set hcopypscolor = 0

```

```
set color0 = rgb:f/f/f
set color1 = rgb:/1/1/1
set color2 = rgb:f/0/0
set color3 = rgb:0/0/f
set color4 = rgb:0/f/0
```

## 4 Experiment completion status

Completed everything in Lab but the ideality factor calculation wee wrong as I forgot to consier non zero  $I_L$

## 5 Questions for reflection

Please see my Design and Simulation Result sections for some answers to questions.  
Overall, the lab was good. Again reports took the most of my time.  
Thanks!